



- (5).two impedances  $5+j5$  and  $5-j5$  ohms are connected in parallel the combined impedance is  
 (a)  $10+j0$  (b)  $2.5-j2.5$  (c)  $5+j0$  (d) 10
- (6).the period of sine wave is  $1/50$  seconds its frequency is  
 (a) 25hz (b) 50 hz (c)100 hz (d)  $16\frac{1}{3}$  hz
- (7).if absolute potential of A point a is 10 volt and that of point B is -5 volt,  $V_{BA}$  will be  
 (a) +15 volt (b) -15 volt (c) 5 volt (d) -5 volt

- Q.2 (A). Assuming the resistivity of copper to be  $1.7 \times 10^{-6}$  ohm.cm . Find the resistance of copper wire of cross section  $1 \text{ mm}^2$  and length 10 meters. Also state the value of the resistance of copper wire if the cross sectional area is made four times keeping the same volume ( $1 \times 1000 \text{ mm}^3$ ) 07
- (B). In a Wheatstone Bridge circuit ,each branch is of 18 ohms and Galvano Meter resistance is also 18 ohms. Find out current delivered by 18 Volt source of the same bridge. 07
- Q3. (A). Explain Coulomb's law. And explain electric potential, equipotential surfaces and electrical field. 07
- (B). A magnetic core has length of 0.2m., and has 100 turns of coil wound around it. A current of 1.2 Amp.in the coil produces a flux density of  $0.18 \text{ webers/m}^2$  in the core. What is the relative permeability of the core materials? 07
- Q.4 (A). Explain  
 (i) Hysteresis loss (ii) Eddy Current Loss 07
- (B). Two coils A and B are mutually coupled so that 55% of the flux of Coil A links Coil B. It is found that current of 2A produces a flux of 0.04 mWb in coil A while the same current in B creates in it flux of 0.05 mWb. If Number of turns are 1000 and 13000 respectively Find  $L_A$  and  $L_B$  of coil A & B respectively(b) Mutual inductance (C) coefficient of coupling. 07
- Q.5 (A) Give comparison of electric circuit and magnetic circuit. 07
- (B) A 10 ohm resistor is connected to 200 Volt sinusoidal 50 Hz supply. Find the peak, rms and average values of the current and also find power dissipated in resistor. 07
- Q.6 (A) State relation between line value and phase value of voltage and current for  
 (i) balanced star connected load.  
 (ii) balanced delta connected load. 07
- (B) What is the purpose of structure earthing? Discuss pipe and plate type earthings. 07
- Q.7 (A) With neat circuit diagram explain working of fluorescent lamp. 07
- (B) Explain the process of charging & discharging of lead acid cell. OR Explain fuel cell in brief. 07