

GUJARAT TECHNOLOGICAL UNIVERSITY
B.E. Sem-I/II Examination June-July 2011

Subject code: 110005

Subject Name: Element of Electrical Engineering

Date: 28/06/11

Total Marks: 70 Time: 10:30 am to 1:00pm

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain the factors affecting the resistance of a conducting material. **03**
- (b) An alternating voltage of $v = 100\sin(376.8 t)$ is applied to a coil having resistance 6Ω and inductance of 21.22 mH . **05**
Determine (i) Current through the coil
(ii) Power dissipated in the coil
- (c) The waveform for instantaneous power in ac circuit is resolved into two component, i.e. $p(t)=p_1(t)+p_2(t)$. Plots of both components are shown in fig no1 . Calculate magnitude of total real power and magnitude of total reactive power (write unit also). **06**
- Q.2** (a) Explain charging and discharging of a capacitor, C, through a resistor, R, with neat sketch and derive the equation $V_c = V (1 - e^{-t/RC})$. Assume that the R-C series circuit is connected across a d.c supply of voltage V. **07**
- (b) A parallel plate capacitor has plates of area 2 m^2 spaced by three slabs of different materials .The relative permittivity are 2,3 and 6 and thickness are 0.4, 0.6 and 1.2 mm respectively. Calculate the equivalent capacitance and electric stress in each material when the applied voltage is 1000 V. **07**
- OR**
- (b) A ring has a mean diameter of 21 cm and a cross sectional area of 10 cm^2 . The ring is made up of semi circular sections of cast iron and cast steel, with joint having reluctance equal to an air gap of 0.2 mm. Find the amp-turns required to produce a flux of $8 \times 10^{-4} \text{ wb}$. The relative permeability of cast steel and cast iron are 800 and 166 respectively. Neglect fringing and leakage effect **07**
- Q.3** (a) State and explain self inductance (L). Derive expression of co-efficient of mutual coupling between two coils having self inductances of L_1 and L_2 . **06**
- (b) Explain magnetic hysteresis **04**
- (c) Prove that the average power consumption in a pure inductive or capacitive circuit is zero. **04**
- OR**
- Q.3** (a) A balanced three phase supply is given to a star connected load. Give proof of two wattmeter method for this system. State demerits of this method. **06**
- (b) Derive the equation of energy stored in a magnetic field. **04**
- (c) An alternating current having an equation $I = 141.4\sin 314t$. **04**

Find: (i) Frequency (ii) R.M.S. Value (iii) Average Value
 (iv) An instantaneous value of current when 't' is 2 ms.

- Q.4 (a)** State and Explain plate and pipe earthing with neat diagram. **07**
(b) General guideline for wiring of domestic installation with neat sketch for position of equipment. **07**

OR


- Q.4 (a)** Explain with diagram different types of illumination scheme. **07**
(b) Explain with neat sketch construction and working of lead acid battery **07**

- Q.5 (a)** Explain with neat sketch general construction of cable. **05**
(b) With necessary diagram derive the formula for star to delta and delta to star transformation. **05**

- (c)** A balanced three phase power supply is connected to a balanced load. Derive the expression of instantaneous power of phase A, $p_a(t)$. Obtain expression of $p(t)$, where $p(t)$ is summation of instantaneous powers of all three phases. assume that $v_a(t) = V_m \sin \omega t$ and $i_a(t) = I_m \sin(\omega t - \Phi)$. **04**

OR

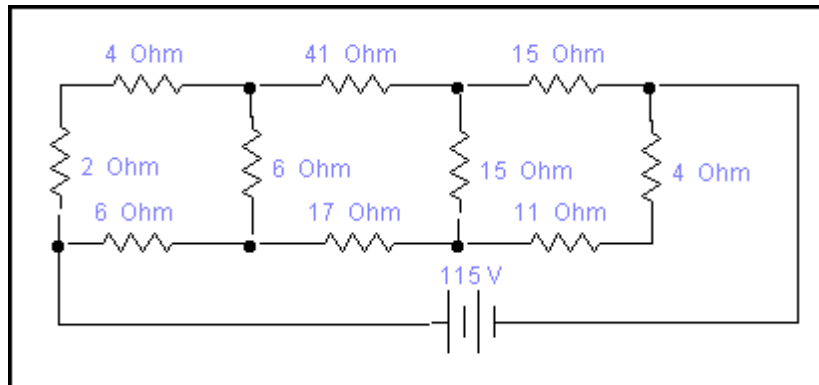- Q.5 (a)** Determine the current in 17Ω resistor in the network shown in Figure **07**



- (b)** Give comparison of series and parallel resonance in R-L-C A.C circuit. Derive expression of quality factor, Q for series R-L-C circuit. **07**

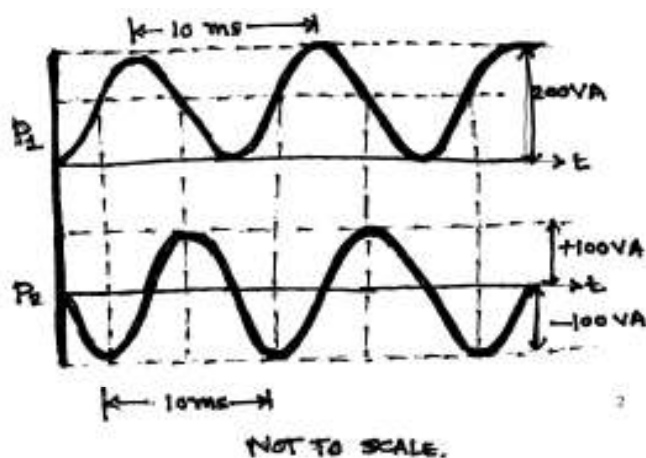


Figure 1
