

GUJARAT TECHNOLOGICAL UNIVERSITY

B.E. Sem-III Remedial Examination May 2011

Subject code: 130902**Subject Name: Analog & Digital Electronics****Date: 27-05-2011****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) What are the feedback configurations? Draw an Op-amp circuit with voltage series feedback and Derive an expression for it., **07**
- (b) Draw the circuit for dual input balanced output differential amplifier using constant current bias circuit. Why current mirror circuit preferred to constant current bias for differential amplifier **07**

- Q.2** (a) Draw and Explain the use of op-amp as a zero crossing detector **07**
- (b) What do you mean by input offset voltage? Draw and explain offset voltage compensating network **07**

OR

- (b) Sketch the circuit of Op-amp as Differentiator and explain with necessary waveforms. **07**

- Q.3** (a) Sketch the diagram of 555 timers as an astable multivibrator having 50% duty cycle. Explain it's working and derive equation for frequency of output waveform. **07**
- (b) Discuss the main features of IC 78 and 79 series voltage regulators. **07**

OR

- Q.3** (a) (i) $(105.15)_{10} = (\quad)_2$ **07**
(ii) $(378.93)_8 = (\quad)_2$
(iii) $(2598.675)_{10} = (\quad)_H$
(iv) $(1100.10)_2 - (111.01)_2 = \underline{\hspace{2cm}}$
(v) $(756.603)_8 = (\quad)_H$
(vi) Subtract with unsigned binary no using 2's complement of subtrahend : 11010 - 10000
(vii) Perform the decimal subtraction in the 8421 BCD code :
206.7-147.8

- (b) Realize Exclusive OR gate using NAND logic and NOR logic. **07**

- Q.4** (a) List the various logic families available and explain in brief the specifications of Digital IC'S. **07**

- (b) Describe the operation performed by following circuits in brief (1) Full Adder (2) Parallel Adder **07**

OR

- Q.4** (a) Minimize the following Boolean expression using K-map and realize it using universal logic gates. **07**
 $Y = \sum m (0,1,2,3,5,7,8,9,10,12,13)$

- (b) What is Multiplexer? Explain basic n input multiplexer with necessary logic diagrams and truth table. List some applications of Multiplexer. **07**
- Q.5** (a) Explain in detail the working of Master-Slave J-K flip-flop **07**
(b) With the help of neat circuit diagram explain the working of: **07**
- (1) A two input TTL NAND gate.
(2) A two input CMOS NOR gate.
- OR**
- Q.5** (a) Write short notes on **10**
(i) Parallel in Serial out shift register
(ii) Binary ripple counter
(b) Compare the CMOS and TTL logic. **04**
