

GUJARAT TECHNOLOGICAL UNIVERSITY
B. E. - SEMESTER – III • EXAMINATION – WINTER 2012

Subject code: 130902**Date: 04-01-2013****Subject Name: Analog and Digital Electronics****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw the equivalent circuit with significance of each component of a practical OP-AMP. **07**
 (b) List and Discuss all ideal characteristics of an Op Amp. **07**
- Q.2** (a) Explain voltage follower and inverter using Op- Amp. **07**
 (b) Draw functional block diagram of IC 555 & discuss function of each pin. **07**
- OR**
- (b) Explain integrator with its frequency response. **07**
- Q.3** (a) Explain the Universal Gate and build up AND, OR and NOT using NAND and NOR gate. **07**
 (b) Derive Full Adder with the help of necessary truth table, K- Map. Also express in AOI logic diagram. **07**
- OR**
- Q.3** (a) Derive Full Subtractor with the help of necessary truth table, K- Map. Also express in AOI logic diagram. **07**
 (b) Do as directed **07**
 1) $(3F8)_{16} + (5B3)_{16} = (\quad)_{16}$
 2) $(231.23)_4 = (\quad)_{10}$
 3) $(111101100)_2 = (\quad)_8$
- Q.4** (a) Define the following general characteristics of logic families. **07**
 (i) Propagation Delay (ii) Noise Margin (iii) Fan-in
 (iv) SOP (v) POS(vi)Fan-Out (vii) Power Dissipation
 (b) 1) Subtract with unsigned binary no using 2's complement of subtrahend **07**
 $x=1010100, y=1000011$, perform $x-y$
 2) Subtract with unsigned binary no using 10's complement of subtrahend
 $x=3250, y=72532$, perform $x-y$.
- OR**
- Q.4** (a) Simplify the following **07**
 1) $xy + xyz + xyz' + x'yz$
 2) $x + x'y + xy'$
- Q.4** (b) Give classification of registers. Discuss 4 – bit buffer register using D – flip flop **07**
- Q.5** (a) i) Minimize the following Boolean expression using K-map. $Y = \sum m(0,1,4,8,9,10)$ **07**
 ii) Discuss multiplexers with suitable diagram
 (b) Explain the working of Master-Slave J-K flip-flop **07**
- OR**
- Q.5** (a) Define decoders, encoder and de-multiplexer Give application of each **07**
 (b) State and explain the triggering methods for a T- flip flop. **07**
