

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER-III • EXAMINATION – WINTER 2013**

**Subject Code: 130902****Date: 28-11-2013****Subject Name: Analog and Digital Electronics****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Define CMRR for a 741C op-amp. **07**  
 A 741C op-amp having the following parameters is connected as non-inverting amplifier:  $R_1 = 1k\Omega$ ,  $R_F = 10k\Omega$ ,  $A = 250 \times 10^3$ ,  $R_i = 1M\Omega$ ,  $R_o = 50\Omega$ ,  $f_0 = 5Hz$ , supply voltages =  $\pm 15V$ , output voltage swing =  $\pm 13V$ .  
 Compute the values of  $A_F$ ,  $R_{iF}$ ,  $R_{oF}$ ,  $f_F$  and  $V_{oot}$ .
- (b)** Discuss Slew Rate with reference to 741C op-amp. **07**
- Q.2 (a)** State and prove De Morgan's theorems. **07**  
**(b)** Do as directed: **07**
- (i)  $(4F7.A8)_{16} = ( \quad )_8$     (ii)  $(420.6)_{10} = ( \quad )_8$   
 (iii)  $(F297)_{16} = ( \quad )_2$     (iv)  $(2EB7)_{16} = ( \quad )_{10}$   
 (v)  $(452)_{10} = ( \quad )_{16}$     (vi)  $(10110)_2 = ( \quad )_{16}$   
 (vii)  $(2035)_8 = ( \quad )_{16}$
- OR**
- (b)** Reduce the following using K-map: **07**
- a.  $\Sigma m (5,6,7,9,10,11,13,14,15)$   
 b.  $\Pi M (1,2,3,5,6,7,8,9,12,13)$
- Q.3 (a)** Describe the working of an integrator circuit with relevant diagrams. **07**  
**(b)** Explain the working of a summing and averaging amplifier when connected in inverting mode. **07**
- OR**
- Q.3 (a)** Discuss the working of wein bridge oscillator. **07**  
**(b)** Write a short note on Zero Crossing Detector. **07**
- Q.4 (a)** Explain the working of JK master slave flip-flop. **07**  
**(b)** Discuss the applications of flip-flops. **07**
- OR**
- Q.4 (a)** Describe the working of look-ahead-carry adder. **07**  
**Q.4 (b)** Explain in brief the working of parity checkers. **07**
- Q.5 (a)** Discuss voltage regulator LM317. **07**  
**(b)** Discuss working of IC555 with function of each pin. **07**
- OR**
- Q.5 (a)** Describe the basic building blocks of PLL. **07**  
**(b)** Define: **07**
- (i) set up time    (ii) hold time    (iii) preset    (iv) clear    (v) fan in    (vi) fan out  
 (vii) propagation delay time

\*\*\*\*\*