

GUJARAT TECHNOLOGICAL UNIVERSITY**B.E. Sem-III Regular / Remedial Examination December 2010****Subject code: 130902 Subject Name: Analog and Digital Electronics.****Date: 15 /12 /2010****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1 (a)** Draw the equivalent circuit with significance of each component of a practical OP-AMP. **07**
- (b)** Define the following characteristics of Practical OP-AMP. **07**
(i) CMRR (ii) PSRR (iii) Slew Rate (iv) Input Offset Voltage.
- Q.2 (a)** Define the following general characteristics of logic families. **07**
(i) Propagation Delay (ii) Noise Margin (iii) Fan-in and Fan-out (iv) Power Dissipation.
- (b)** What are SOP and POS forms of boolean expressions? Minimize the following expression using K-MAP. **07**
 $Y = \sum m(0,1,5,9,13,14,15) + d(3,4,7,10,11)$
- OR**
- (b) (i)** Convert $(0.8)_{10}$ to equivalent binary. **07**
(ii) Convert $(B9F.AE)_{16}$ to equivalent octal.
(iii) Convert $(2003.31)_{10}$ to equivalent hex.
- Q.3 (a)** Draw the circuit of a differentiator using OP-AMP. What are the problems associated with the circuit? How are they overcome? **07**
- (b)** Explain with the help of circuit diagram the basic operation of OP-AMP as a comparator. Also explain the operation of zero cross detector. **07**
- OR**
- Q.3 (a)** Explain the working of an IC-555 as a bistable multivibrator. **07**
- (b)** List out the different performance parameters of a Power Supply. Describe the operation of a LM317 voltage regulator. **07**
- Q.4 (a)** Design a full adder using universal NAND gate. Also explain how four bit combined binary adder and subtractor circuit can be constructed using full adders.? **07**
- (b)** Classify different types of digital to analog converters. With the neat circuit diagram, explain the operation of R-2R ladder digital to analog converter. **07**
- OR**
- Q.4 (a)** With the neat diagram explain the working of decimal to BCD encoder. **07**
- (b)** What is the application of gray code.? Design a binary to gray conversion combinational circuit. **07**
- Q.5 (a)** Distinguish between combinational and sequential circuit. What are the basic difference between truth table and a state table? Also explain the concept of state diagram using suitable example. **07**
- (b)** What is the basic difference between synchronous and asynchronous counter? Design a four bit synchronous up counter using J-K flip flop. **07**
- OR**
- Q.5 (a)** State and explain the triggering methods for a D- flip flop. **07**
- (b)** Classify the various modes of operation of shift registers. Explain the serial in parallel out operation of shift register. **07**
