

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI • EXAMINATION – SUMMER • 2015****Subject Code:160905****Date:12/05/2015****Subject Name:Electrical and Electronic Measurement****Time:10.30am-01.00pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) State the methods for measurement of high resistance and explain any one in detail. **07**
- (b) Explain the following terms, **07**
1. Sensitivity 2. Accuracy 3. Drift 4. Precision 5. Linearity
6. Resolution 7. Stability.
- Q.2** (a) Explain Maxwell's inductance-capacitance bridge with circuit diagram and phasor diagram. Derive the condition for balance. **07**
- (b) Describe sources and null detector used in A.C. bridge **07**
- OR**
- (b) Derive equation for De sauty's bridge for capacitor measurement with diagram. **07**
- Q.3** (a) Draw the circuit of Kelvin's double bridge used for measurement of low resistance. Derive the condition for balance. **07**
- (b) Explain Murray loop test for localization of ground and short circuit fault in cables. **07**
- OR**
- Q.3** (a) Describe the varley loop test for localization of ground and short circuit fault in cables. **07**
- (b) Explain fall of potential method for measurement of earth resistance. **07**
- Q.4** (a) Draw the equivalent circuit and phasor diagram of a current transformer. Derive the expression for ratio and phase angle errors. **07**
- (b) Discuss principle and working of digital LCR meter. **07**
- OR**
- Q.4** (a) Describe the method for determination of B-H curve of magnetic material. **07**
- (b) Explain comparison method of testing of potential transformer. **07**
- Q.5** (a) Explain Harmonic distortion analyser. **07**
- (b) Explain constructional features and working of flux meter. **07**
- OR**
- Q.5** (a) Discuss applications of spectrum analyser. **07**
- (b) State the requirements of a good instrumentation amplifier. **07**
