

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Semester -III Remedial Examination April - 2010****Subject code: 331102****Subject Name: Digital Electronics****Date: 21/ 04 /2010****Time: 03.00 pm – 05.30 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version Authentic

- Q.1** (a) Describe the terms: resolution, accuracy, conversion speed and sampling speed, for A/D converter. **04**
- (b) Describe the Successive Approximation A/D converter in detail. **06**
- (c) Explain RAM and ROM in brief. **04**
- Q.2** (a) Convert the following decimal number in Binary, Octal and Hexadecimal number, **07**
- (i) 1024 (ii) 422.48
- (b) Do the following subtractions using 2's complement, **07**
- (i) 101100 – 111111 (ii) 7C – FE (iii) 101 - 11010
- OR**
- (b) Do the following operations, **07**
- (i) 1011×101 (ii) $1111 \div 0011$ (iii) 1011×111
- Q.3** (a) Discuss NAND, NOR, EX-OR, EX-NOR gates with the help of symbol, operation and truth table. **07**
- (b) Explain two inputs NAND gate circuit of TTL and CMOS families. **07**
- OR**
- Q.3** (a) Simplify the following functions using karnaugh map, **07**
- (i) $F(a,b,c,d) = \sum(3,5,6,7,11,13,14,15)$
- (ii) $F(x,y,z) = \sum(2,3,4,5,7)$
- (b) Prove the following **07**
- (i) $A'BC + AB'C + ABC' + ABC = BC + AC + AB$
- (ii) $AB + BC(B + C) = B(A+C)$
- (iii) $((AB'C)' + (ACD)' + (BC'))' = AB'CD$
- Q.4** (a) (a1) Convert the following Gray codes into Binary codes, **03**
- (i) 1001101 (ii) 111111001
- (a2) Explain Full adder circuit in detail. **04**
- (b) Discuss 3×8 Decoder and 8×3 Encoder circuits. **07**
- OR**
- Q. 4** (a) What is parity bit? Explain even parity generator and checker circuits. **07**
- (b) Explain Multiplexer circuit with appropriate example and discuss its applications. **07**
- Q.5** (a) Explain operation of J-K flip flop using circuit and truth table. **07**
- (b) Discuss the application of flip flops in brief. **07**
- OR**
- Q.5** (a) Explain 4-bit asynchronous binary counter with necessary diagram. **07**
- (b) Discuss the different types of shift registers with necessary diagram. **07**

પ્રશ્ન-૧	અ	A/D કન્વર્ટર માટે એક્ચ્યુરસી, રીઝોલ્યુશન, કન્વર્ઝન સ્પીડ તથા સેમ્પલીંગ સ્પીડનું વર્ણન કરો	04
	બ	સક્સેસીવ એપ્રોક્ષીમેશન બળમ કન્વર્ટરનું સવિસ્તાર વર્ણન કરો.	06
	ક	RAM તથા ROM વિશે ટૂંકમાં સમજાવો.	04
પ્રશ્ન-૨	અ	નીચે દર્શાવેલ ડેસીમલ નંબરને બાઇનરી, ઓક્ટલ અને હેક્ષાડેસીમલ નંબરમાં ફેરવો. (i) 1024 (ii) 422.48	07
	બ	2's કોમ્પ્લીમેન્ટનો ઉપયોગ કરી નીચે દર્શાવેલની બાદબાકી કરો: (i) 101100 - 111111 (ii) 7C - FE (iii) 101 - 11010	07
		અથવા	
	બ	નીચે દર્શાવેલ ઓપરેશન કરો : (i) 1011 × 101 (ii) 1111 ÷ 0011 (iii) 1011 × 111	07
પ્રશ્ન-૩	અ	NAND, NOR, EX-OR, EX-NOR ગેટ વિશે સીમ્બોલ, ઓપરેશન અને ટ્રુથ ટેબલ સાથે વર્ણન કરો.	07
	બ	બે ઇનપુટ NAND ગેટનું TTL તથા CMOS ફેમીલીની આકૃતિ સાથે વર્ણન કરો.	07
		અથવા	
પ્રશ્ન-૩	અ	નીચેનાનું કાર્નોપ મેપનો ઉપયોગ કરી સીમ્પ્લીફાય કરો : (i) $F(a,b,c,d) = \sum(3,5,6,7,11,13,14,15)$ (ii) $F(x,y,z) = \sum(2,3,4,5,7)$	07
	બ	નીચેનાને સાબીત કરો : (i) $A'BC + AB'C + ABC' + ABC = BC + AC + AB$ (ii) $AB + BC(B + C) = B(A+C)$ (iii) $((AB'C)' + (ACD)' + (BC'))' = AB'CD$	07
પ્રશ્ન-૪	અ	(૧) નીચેના ગ્રે કોડનું બાઇનરી કોડમાં રૂપાંતર કરો : (i) 1001101 (ii) 111111001	03
		(૨) કુલ એડર સર્કીટનું સવિસ્તાર વ્ણન કરો.	04
	બ	3×8 Decoder અને 8×3 Encoder સર્કીટનું વર્ણન કરો.	07
		અથવા	
પ્રશ્ન-૪	અ	પેરીટી બીટ એટલે શું? ઇવન પેરીટી જનરેટર તથા ચેકર સર્કીટ સમજાવો.	07
	બ	મલ્ટીપ્લેક્ષર વિશે જુરી ઉદાહરણ આપી વર્ણન કરો તથા તેના ઉપયોગ વિશે સમજાવો.	07
પ્રશ્ન-૫	અ	J-K flip flop વિશે સર્કીટ તથા ટ્રુથ ટેબલ સાથે સમજાવો.	07
	બ	flip flop ના ઉપયોગો ટૂંકમાં સમજાવો.	07
		અથવા	
પ્રશ્ન-૫	અ	જરુરી આકૃતિ સાથે 4-bit અસીંક્રોનશ બાઇનરી કાઉન્ટર સમજાવો.	07
	બ	જરુરી આકૃતિ સાથે જુદા જુદા પ્રકારના શિફ્ટ રજિસ્ટરની ચર્ચા કરો.	07
