

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Sem-IV Examination July 2010****Subject code: 342401****Subject Name: Elements of Power Electronics****Date: 06 / 07 / 2010****Time: 10:30am-1:00pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- Q.1** (a) Compare general purpose diode, fast recovery diode and schottky diode **07**
 (b) List the name of power semiconductor devices. Give the Power Electronics converters classification with their applications **07**
- Q.2** (a) Explain construction and draw the V-I characteristics of UJT & DIAC. **07**
 (b) Explain two transistor analogy of SCR and explain why silicon material used in thyristor. Define the term latching & holding current. **07**
- OR**
- (b) Explain briefly, what happens in a thyristor when the rate of rise of load current and rate of rise of anode to cathode voltage are excessive? **07**
- Q.3** (a) Draw UJT relaxation oscillator circuit with waveform and explain it's working **07**
 (b) Draw R. C. Phase shift network and derive equation for it. **07**
- OR**
- Q.3** (a) Draw PUT Triggering circuit with waveform and write it's operation. **07**
 (b) List the turn-on methods of SCR. Explain any one with circuit diagram and waveform using pulse transformer. **07**
- Q.4** (a) What Is IGBT ? Sketch the equivalent circuit and transfer characteristics of an IGBT. **07**
 (b) How does GTO differ from a conventional thyristor ? Give the advantages of an RCT over a conventional thyristor. **07**
- OR**
- Q. 4** (a) Explain the switching characteristics of an IGBT. **07**
 (b) Compare power MOSFETs with power BJTs. **07**
- Q.5** (a) Explain the operation of a single – thyristor half wave controlled rectifier with waveform. **07**
 (b) Draw circuit diagram for fixed DC to variable DC conversion and explain working. **07**
- OR**
- Q.5** (a) Define function of snubber circuit. Draw snubber circuit for SCR and Transistor. **07**
 (b) Draw circuit diagram for fixed AC to variable AC conversion and explain working. **07**

- પ્રશ્ન-૧ અ સામાન્ય ડાયોડ, ફાસ્ટ રીકવરી ડાયોડ અને સ્કોટી ડાયોડ ની સરખામણી કરો. 07
 બ પાવર સેમીકંડક્ટર ડિવાઈસના નામો આપો. પાવર ઇલેક્ટ્રોનિક્સ કન્વર્ટરનું વર્ગિકરણ કરી તેઓની ઉપયોગીતાઓ જણાવો. 07
- પ્રશ્ન-૨ અ UJT અને DIAC ની V-I લાક્ષણિકતા દોરી તેમની રચના જણાવો. 07
 બ SCR માટે બે ટ્રાંસિસ્ટર એનાલોજી સમજાવો. SCR માં સીલીકોન મટીરીયલ શા માટે વપરાય છે. લેચીંગ કરંટ અને હોલ્ડીંગ કરંટ વ્યાખ્યાતીત કરો. 07
 અથવા
 બ SCR માટે રેટ ઓફ રાઈજ ઓફ લોડ કરંટ અને રેટ ઓફ રાઈજ ઓફ એનોડ ટુ કેથોડ વોલ્ટેજ વધી જાય તો શું થાય તે સમજાવો. 07
- પ્રશ્ન-૩ અ UJT રીલેક્સેશન ઓસિલેટરનો પરીપથ વેવફોર્મ સાથે દોરી તેનું કાર્ય સમજાવો. 07
 બ RC ફેઈસ સીફ્ટ નેટવર્ક પરીપથ દોરી તેનું સુત્ર મેળવો. 07
 અથવા
- પ્રશ્ન-૩ અ PUT ટ્રીગર પરીપથ વેવફોર્મ સાથે દોરી તેનું કાર્ય સમજાવો. 07
 બ SCR ચાલુ કરવાની પદ્ધતીઓના નામો આપો. પલ્સ ટ્રાન્સફોરમર ઉપયોગ કરીને ગમે તે એક પરીપથ વેવફોર્મ સાથે દોરો. 07
- પ્રશ્ન-૪ અ IGBT શું છે ? IGBT માટે સમકક્ષ પરીપથ અને ટ્રાંસફર લાક્ષણિકતા દોરો. 07
 બ સામાન્ય SCR થી GTO કેવી રીતે અલગ પડે છે? સામાન્ય SCR કરતા RCT ના ફાયદાઓ જણાવો. 07
 અથવા
- પ્રશ્ન-૪ અ IGBT માટેની સ્વીચીંગ લાક્ષણિકતાઓ સમજાવો. 07
 બ MOSFETs અને પાવર BJT's ની સરખામણી કરો. 07
- પ્રશ્ન-૫ અ એક SCR આધારીત હાફ વેવ કંટ્રોલ રેક્ટીફાયર વેવફોર્મ સાથે દોરી સમજાવો. 07
 બ ફીક્સ DC થી વેરીએબલ DC કન્વર્જન માટેનો પરીપથ દોરી સમજાવો. 07
 અથવા
- પ્રશ્ન-૫ અ સ્નબર સર્કિટ નું કાર્ય જણાવો. SCR અને ટ્રાંસિસ્ટર માટે સ્નબર સર્કિટ દોરો. 07
 બ ફીક્સ AC થી વેરીએબલ AC કન્વર્જન માટેનો સર્કિટ પરીપથ દોરો અને કાર્ય સમજાવો. 07
