

GUJARAT TECHNOLOGICAL UNIVERSITY**DIPLOMA ENGG.- I/IInd SEMESTER-EXAMINATION -JUNE/JULY- 2012****Subject code: 320017****Date: 19/06/2012****Subject Name: Electronics Devices And Circuits - I****Time: 10:30 am – 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic

- Q.1** (a) With the help of band theory explain difference between conductor ,semiconductor and insulator. **06**
 (b) Explain Full wave Rectifier circuit with necessary input & output waveforms. Give the difference between half wave and full wave rectifier circuit. **08**
- Q.2** (a) What is extrinsic semiconductor? Explain P-type and N-type semiconductor. **07**
 (b) How P-N junction is formed ? Draw and Explain characteristics of PN junction diode **07**
- or**
- (b) Why filter circuit are necessary? List various filter circuits and explain any one of them. **07**
- Q.3** (a) What is biasing ? State different methods of transistor biasing and explain any one of them. **07**
 (b) With the help of diagram explain input and output characteristics of CE amplifier **07**
- or**
- Q.3** (a) Explain the frequency response of RC coupled amplifier . **06**
 (b) What is hybrid parameter ? Draw and Explain h-parameter model of CE amplifier. **08**
- Q.4** (a) Describe the working of NPN transistor. **05**
 (b) Explain in brief the working of diode clipper and clamper circuits. **05**
 (c) Define α and β of the transistor and obtain relationship between them. **04**
- or**
- Q. 4** (a) Compare between CE,CB and CC configuration of transistor amplifier. **05**
 (b) Draw and explain working of diode voltage doubler circuit. **05**
 (c) Explain in brief Opto coupler and Opto isolator **04**
- Q.5** (a) Explain in brief Uninterrupted power supply (UPS) **05**
 (b) Explain in brief series voltage regulator circuit. **05**
 (c) Draw the circuits of three terminal voltage regulator. **04**
- or**
- Q.5** (a) Explain in brief switch mode power supply (SMPS) **05**
 (b) Explain in brief shunt voltage regulator circuit. **05**
 (c) Explain the working of the Darlington pair with circuit diagram **04**
- પ્ર.૧ (અ) બેન્ડ થીયરી ની મદદ થી કન્ડક્ટર, સેમિકન્ડક્ટર અને ઇન્સુલેટર વચ્ચે **૦૬**

નો તફાવત સમજાવો.

- (બ) ઇનપુટ અને આઉટપુટ વેવફોર્મ સાથે કુલ વેવ રેક્ટીફાયર સર્કીટ સમજાવો. હાફ વેવ અને કુલ વેવ રેક્ટીફાયર સર્કીટ વચ્ચે ના તફાવત આપો. ૦૮
- પ્ર.૨ (અ) એસ્ટ્રીન્સિક સેમિકન્ડક્ટર એટલે શું ? P-ટાઇપ અને N- ટાઇપ સેમિકન્ડક્ટર સમજાવો ૦૭
- (બ) P-N જંક્શન ની રચના કેવી રીતે થાય છે ? PN જંક્શન ડાયોડ ની લાક્ષણિકતા સમજાવો. ૦૭
- અથવા
- (બ) ફિલ્ટર સર્કીટ ની શું જરૂરીયાત છે ? વિવિધ પ્રકાર ના ફિલ્ટર સર્કીટો ની યાદી તૈયાર કરો અને તેમની કોઇ પણ એક સર્કીટ સમજાવો. ૦૭
- પ્ર.૩ (અ) બાયસિંગ એટલે શું ? ટ્રાન્સિસ્ટર બાયસિંગ માટે ની પધ્ધતીઓના નામ આપો અને તેમની કોઇ પણ એક પધ્ધતી સમજાવો ૦૭
- (બ) આકૃતિ ની મદદ થી CE એમ્પ્લિફાયર ની ઇનપુટ અને આઉટપુટ લાક્ષણિકતા સમજાવો. ૦૭
- અથવા
- પ્ર.૩ (અ) RC કપ્લ એમ્પ્લિફાયર નો ફ્રીક્વન્સી રીસ્પોન્સ સમજાવો. ૦૬
- (બ) હાઇબ્રિડ પેરામીટર એટલે શું? CE એમ્પ્લિફાયર માટે h-પેરામીટર મોડેલ દોરો અને સમજાવો. ૦૮
- પ્ર.૪ (અ) NPN ટ્રાન્સિસ્ટર નું કાર્ય ટુંકમાં સમજાવો. ૦૫
- (બ) ડાયોડ ક્લિપર અને ક્લેમ્પર સર્કીટો નું કાર્ય ટુંકમાં સમજાવો. ૦૫
- (ક) ટ્રાન્સિસ્ટર માટે α અને β ની વ્યાખ્યા આપો અને તેમના વચ્ચે નો સબંધ મેળવો. ૦૪
- અથવા
- પ્ર.૪ (અ) ટ્રાન્સિસ્ટર એમ્પ્લિફાયર ની CE, CB અને CC કનફિગરેશન સરખાવો. ૦૫
- (બ) ડાયોડ વોલ્ટેજ ડ્રબ્લર સર્કીટ દોરો અને તેનું કાર્ય સમજાવો. ૦૫
- (ક) ઓપ્ટો કપ્લર અને ઓપ્ટો આઇસોલેટર ટુંકમાં સમજાવો. ૦૪
- પ્ર.૫ (અ) અનઇન્ટરપ્ટેડ પાવર સપ્લાય (UPS) ટુંકમાં સમજાવો. ૦૫
- (બ) સિરીઝ વોલ્ટેજ રેગ્યુલેટર સર્કીટ ટુંકમાં સમજાવો. ૦૫
- (ક) ટ્રણ ટર્મિનલ વોલ્ટેજ રેગ્યુલેટર સર્કીટો દોરો. ૦૪
- અથવા
- પ્ર.૫ (અ) સ્વિચમોડ પાવર સપ્લાય (SMPS) ટુંકમાં સમજાવો. ૦૫
- (બ) શન્ટ વોલ્ટેજ રેગ્યુલેટર સર્કીટ ટુંકમાં સમજાવો. ૦૫
- (ક) સર્કીટ ડાયાગ્રામ ની મદદ થી ડાર્લીંગ્ટન પેર નું કાર્ય સમજાવો. ૦૪
