

**GUJARAT TECHNOLOGICAL UNIVERSITY****DIPLOMA ENGG.- III<sup>rd</sup> SEMESTER-EXAMINATION – MAY/JUNE- 2012****Subject code: 331102****Date: 29/05/2012****Subject Name: Digital Electronics****Time: 02:30 pm – 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic

- Q.1** (a) Perform following : **07**  
 (i)  $(7A6)_{16} = ( \quad )_2 = ( \quad )_8 = ( \quad )_{10}$   
 (ii)  $(256)_{10} = ( \quad )_{16} = ( \quad )_8 = ( \quad )_2$
- (b) Perform following : **07**  
 (i)  $(101.1)_2 \times (1.01)_2 + (101.101)_2 = ( \quad )_2 = ( \quad )_{10}$   
 (ii)  $(8C)_{16} + (11)_8 + (100)_2 = ( \quad )_2 = ( \quad )_{10}$   
 (Show the calculation performed for filling the blanks)
- Q.2** (a) State and prove D' Morgan's theorem. **07**  
 (b) Draw the symbols of following gates: **07**  
 (i) AND (ii) NOT (iii) NAND (iv) EX-OR  
 (v) BUBBLED OR GATE
- OR**
- (b) Draw the truth table of following gates : **07**  
 (i) OR (ii) NOT (iii) NOR (iv) EX-OR  
 (v) UNIVERSAL NAND GATE
- Q.3** (a) Explain terms : **07**  
 (i) Setup time (ii) +Ve Logic (iii) –Ve Logic (iv) Hold time  
 (v) Saturation delay (vi) Propagation delay
- (b) Simplify the following using Boolean algebra : **07**  
 (i)  $Y = ABC + \overline{A}BC + A\overline{B}C$   
 (ii) Show that:  $AB + \overline{A}BC + \overline{B}C + \overline{C}A = 1$
- OR**
- Q.3** (a) (1) Define a combinational system ? How does it differ from a sequential system? **07**  
 (2) Discuss the advantages and disadvantages CMOS ICs OVER TTL ICs
- (b) Draw TTL NAND gate circuit and Explain the working. **07**
- Q.4** (a) Draw the logic diagram of FULL\_ADDER using two HALF\_ADDER and OR gate **07**  
 (b) What is the importance of multiplexer? Draw and Explain logic diagram of 4 to 1 line multiplexer. **07**
- OR**
- Q.4** (a) Reduce the following expression using karnaugh map. **07**  
 (i)  $F = \sum m(0, 2, 6, 10, 11, 12, 13)$  Don't care  $d(3, 4, 5, 14, 15)$

- (ii)  $F = \sum m(1,2,6,7,8,13,14,15)$  Don't care  $d(3,5,12)$
- Q.5 (b) What is parity? Explain parity generator. State application. **07**
- (a) Explain the working of a ring counter. **07**
- (b) Explain the working of JK flip-flop with the help of Logic circuit and truth table. Why master slave operation is required? **07**
- OR**
- Q.5 (a) (1) Explain characteristics of ROM, PROM and EPROM. **07**
- (2) Discuss 3×8 DECODER and 8×3 ENCODER circuit
- (b) Explain 4 bit a R-2R ladder digital to Analog converter. Discuss following specification for D/A converter. **07**
- (i) Accuracy (ii) Resolution

\*\*\*\*\*

- પ્રશ્ન-૧ અ નીચેનાની ગણતરી કરો. **07**
- (i)  $(7A6)_{16} = ( )_2 = ( )_8 = ( )_{10}$
- (ii)  $(256)_{10} = ( )_{16} = ( )_8 = ( )_2$
- બ નીચેનાની ગણતરી કરો. **07**
- (i)  $(101.1)_2 \times (1.01)_2 + (101.101)_2 = ( )_2 = ( )_{10}$
- (ii)  $(8C)_{16} + (11)_8 + (100)_2 = ( )_2 = ( )_{10}$
- (ઉપરોક્તની ગણતરી કરીને ખાલી જગ્યા પુરો.)

- પ્રશ્ન-૨ અ ડી-મોર્ગન થીયરમ લખો અને સાબિત કરો. **07**
- બ નીચેના ગેટ ના સીમ્બોલ દોરો. **07**
- (i) AND (ii) NOT (iii) NAND (iv) EX-OR
- (v) BUBBLED OR GATE
- અથવા
- બ નીચેના ગેટનું ટ્રુથ ટેબલ સાથે વર્ણન કરો. **07**
- (i) OR (ii) NOT (iii) NOR (iv) EX-OR
- (v) UNIVERSAL NAND GATE

- પ્રશ્ન-૩ અ નીચેનાની વ્યાખ્યા આપો. **07**
- (i) Setup time (ii) +Ve Logic (iii) -Ve Logic (iv) Hold time
- (v) Saturation delay (vi) Propagation delay
- બ બુલિયન એલ્જીબ્રા ની મદદથી નીચેનાનું સાદું રૂપ આપો **07**
- (ii)  $Y = ABC + \overline{A}BC + A\overline{B}C$
- (ii) દર્શાવો :  $AB + \overline{A}BC + \overline{B}C + AC = 1$

અથવા

- પ્રશ્ન-૩ અ (1) કોમ્પીનેશનલ સીસ્ટમની વ્યાખ્યા આપો? સીકવંશ્યલ સર્કીટ તેનાથી કેવી રીતે જુદી પડે છે તે સમજાવો. **07**
- (2) CMOS ICs અને TTL ICs ના ફાયદા અને ગેર ફાયદા જણાવો.
- બ TTL NAND ગેટ ની આકૃતિ દોરો અને તેનું કાર્ય સમજાવો **07**

પ્રશ્ન-૪

- અ બે HALF\_ADDER અને OR ગેટ ની મદદથી FULL\_ADDER નો લોજિક ડાયાગ્રામ દોરો. 07
- બ Multiplexer નું મહત્વ સમજવો? 4 to 1 line Multiplexer નો લોજિક ડાયાગ્રામ દોરો અને સમજાવો. 07

અથવા

પ્રશ્ન-૪

- અ નીચેનાનું કાર્નોફ મેપનો ઉપયોગ કરી સિમ્પ્લીફાય કરો. 07
- (i)  $F = \sum m(0,2,6,10,11,12,13)$  Don't care  $d(3,4,5,14,15)$
- (ii)  $F = \sum m(1,2,6,7,8,13,14,15)$  Don't care  $d(3,5,12)$
- બ પેરીટી બીટ એટલે શું? પેરીટી જનરેટર સમજાવો. તથા તેના ઉપયોગો લખો. 07

પ્રશ્ન-૫

- અ રીંગ કાઉન્ટર નું કાર્ય સમજાવો. 07
- બ JK flip-flop ની લોજિક સર્કીટ ની મદદથી તેનું કાર્ય તથા ટ્રુથ ટેબલ સમજાવો. માસ્ટર સ્લેવ ઓપરેશન શા માટે જરૂરી છે? 07

અથવા

પ્રશ્ન-૫

- અ (1) ROM, PROM અને EPROM ના લક્ષણો સમજાવો. 07
- (2)  $3 \times 8$  DECODER અને  $8 \times 3$  ENCODER સર્કીટનું વર્ણન કરો.
- બ 4 બીટનું R-2R લેડર D/A કંવર્ટર સમજાવો. D/A કંવર્ટરના સ્પેસીફિકેશનની ચર્ચા કરો. (i) એક્ચ્યુરેસી (ii) રીઝોલ્યુશન 07

\*\*\*\*\*