

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-II • EXAMINATION – SUMMER 2013****Subject Code: 3322402****Date: 15-06-2013****Subject Name: Digital Electronics****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. Convert $(4021)_{10}$ in Binary number.
 2. Convert 10010110 Gray code in Binary code.
 3. Draw digital logic circuit for the equation $Y = A'B + A'B$ Where Y= output and A,B = input
 4. Convert $(BC)_{16}$ in Decimal number.
 5. $(1011)_2 - (1001)_2$ using 1'st compliment method.
 6. Write any two differences between combinational and sequential logic circuits.
 7. Write a truth table for half adder.
 8. Convert Octal $(256)_8$ in Hexadecimal number.
 9. Draw Karnaugh maps for $F = \sum m(0, 3, 4, 5, 7, 9, 12)$ in Sum Of Product (SOP) form.
 10. $(1A)_{16} = (\dots\dots)_2$.
- Q.2** (a) Explain Excess-3 code with suitable example. **03**
OR
- (a) Explain binary to Gray code converter with suitable example. **03**
(b) Give the BCD equivalent for the decimal number $(69.27)_{10}$ **03**
OR
- (b) Perform binary multiplication on following number $101 * 11010$ **03**
(c) Perform following operation $(1E)_{16} + (10)_8 + (111)_2 = (\dots\dots)_{10}$ **04**
OR
- (c) Simplify $Y = AB'C + ABC + A'C$ using Boolean algebra. **04**
(d) Explain Full adder circuit with truth table and logic circuit diagram. **04**
OR
- (d) Explain Half subtractor circuit with truth table and logic circuit diagram. **04**
- Q.3** (a) Explain even parity generator circuit with digital circuit diagram **03**
OR
- (a) Explain 1-bit magnitude comparator with digital circuit diagram. **03**
(b) Simplify equation for the following function using karnaugh map, $F(a,b,c) = \sum(3,5,4,6,7)$ **03**
OR
- (b) Prove the following $AB + BC(B + C) = B(A+C)$ **03**
(c) Using logic gates, draw and explain circuit of 3 X 8 decoder in short. **04**
OR
- (c) Using logic gates draw and explain circuit of 4 X 1 multiplexer in short. **04**
(d) Explain Don't care condition with an example. **04**

	OR	
	(d) State and prove De Morgan's theorem.	04
Q.4	(a) Using NAND gates, realize EXOR gate.	03
	OR	
	(a) Using NOR gate, realize AND gate.	03
	(b) What is sequential circuit? Explain S-R flip flop using truth table and its digital circuit.	04
	OR	
	(b) Explain operation of J-K flip flop using digital circuit and truth table.	04
	(c) Discuss the application of flip flops and multiplexer in brief.	07
Q.5	(a) Draw and explain TTL NAND gate with open collector output in short.	04
	(b) Write full forms of RTL, DTL, TTL, MOS, CMOS logic families and Write a short note on DTL.	04
	(c) Compare CMOS and TTL ICs.	03
	(d) Draw and explain DTL NOR gate circuit in short.	03

ગુજરાતી

પ્રશ્ન. ૧	દશમાંથી કોઈપણ સાતના જવાબ આપો.	૧૪
	૧. $(4021)_{10}$ ને બાઈનરી નંબર સીસ્ટમ મા ફેરવો.	
	૨. ગ્રે કોડ- 10010110 ને બાઈનરી કોડ મા ફેરવો.	
	૩. સમીકરણ $Y = A'B + AB'$ માટે લોજિક સરકીટ દોરો. જ્યાં Y આઉટપુટ અને A, B ઈનપુટ છે.	
	૪. $(BC)_{16}$ ને ડેસીમલ નંબર સીસ્ટમ મા ફેરવો.	
	૫. 1 st કોમ્પ્લીમેન્ટ ની મદદ થી $(1011)_2 - (1001)_2$ શોધો.	
	૬. કોમ્પીનેશનલ અને સીક્વંસીયલ લોજિક સરકીટ વચે ના કોઈપણ બે તફાવત લખો.	
	૭. હાફ એડર માટે ટ્રુથ ટેબલ દોરો.	
	૮. $(256)_8$ ને હેક્ઝાડેસીમલ મા ફેરવો.	
	૯. $F = \sum m(0,3,4,5,7,9,12)$ માટે K-Map સમ ઓફ પ્રોડક્ટ ના ફોર્મ મા દોરો	
	૧૦. $(1A)_{16} = (\dots\dots)_2$.	
પ્રશ્ન. ૨	અ Excess-3 કોડ યોગ્ય ઉદાહરણ આપી સમજાવો.	03
	અથવા	
	અ બાઈનરી માથી ગ્રે કોડ કનવર્ટર યોગ્ય ઉદાહરણ આપી સમજાવો.	03
	બ $(69.27)_{10}$ માટે BCD ઈક્વાવેલેન્ટ શોધો.	03
	અથવા	
	બ આપેલા નંબર માટે બાઈનરી ગુણાકાર કરો. $101 * 11010$	03
	ક આપેલા સમીકરણ માટે જવાબ આપો. $(1E)_{16} + (10)_8 + (111)_2 = (\dots\dots)_{10}$	04

અથવા

- ક સમીકરણ $Y = AB'C + ABC + A'C$ નુ સાદુ રુપ આપો. 0૪
- ડ ટ્રુથ ટેબલ અને લોજીક સરકીટ ની મદદ થી કુલ એડર સમજાવો. 0૪

અથવા

- ડ ટ્રુથ ટેબલ અને લોજીક સરકીટ ની મદદ થી હાફ સબટ્રાક્ટર સમજાવો. 0૪
- પ્રશ્ન. ૩ અ ડીજીટલ સરકીટ ની મદદ થી ઈવન પ્રાયોરીટી જનરેટર સમજાવો. 0૩

અથવા

- અ ડીજીટલ સરકીટ ની મદદ થી 1-બીટ મેઝીનિટ્યુડ જનરેટર સમજાવો. 0૩
- બ કારનોટ મેપ ની મદદ થી $F(a,b,c) = \sum(3,5,4,6,7)$ નુ સમીકરણ સાદુરુપ આપો 0૩

અથવા

- બ $AB + BC(B + C) = B(A+C)$ સાબીત કરો. 0૩
- ક લોજીક ગેટ ની મદદ થી 3 X 8 ડીકોડર સમજાવો. 0૪

અથવા

- ક લોજીક ગેટ ની મદદ થી 4 X 1 મલ્ટીપ્લેક્સર સમજાવો. 0૪
- ડ ડોટ કેર શરત ઉદાહરણ સાથે સમજાવો. 0૪

અથવા

- ડ ડી મોર્ગન થીયરમ લખો અને સાબિત કરો. 0૪
- પ્રશ્ન. ૪ અ NAND ગેટ ની મદદ થી X-OR ગેટ બનાવો 0૩

અથવા

- અ NOR ગેટ ની મદદ થી AND ગેટ બનાવો 0૩
- બ સીક્વંસીયલ સરકીટ શુ છે? ટ્રુથ ટેબલ અને લોજીક સરકીટ ની મદદ થી S-R ફ્લોપ ફ્લોપ સમજાવો. 0૪

અથવા

- બ ટ્રુથ ટેબલ અને લોજીક સરકીટ ની મદદ થી J-K ફ્લોપ ફ્લોપ સમજાવો. 0૪
- ક ફ્લોપ ફ્લોપ અને મલ્ટીપ્લેક્સર ના ઉપયોગો સવિસ્તાર સમજાવો. 0૭
- પ્રશ્ન.૫ અ ઓપન કલેક્ટર આઉટપુટ ધરાવતો TTL NAND દોરો અને સમજાવો 0૪
- બ RTL, DTL, TTL, MOS, CMOS લોજીક ફેમીલી ના પુરા નામ જણાવો અને DTL વિશે ટુક મા સમજાવો. 0૪
- ક CMOS અને TTL IC ને સરખાવો. 0૩
- ડ DTL NOR ગેટ દોરો અને ટુક મા સમજાવો 0૩
