

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING – SEMESTER – II EXAMINATION – SUMMER-2015

Subject Code:3321102

Date: 10 / 06/2015

Subject Name: ELECTRONIC NETWORKS

Time: 10:30 am to 1:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

- Q.1** Answer any seven out of ten. **14**
1. Define passive network.
 2. Define non- linear network.
 3. Define lumped network.
 4. Define bilateral network.
 5. Define asymmetrical network.
 6. Statement of KCL.
 7. Define Bandwidth.
 8. Definition of Q (quality factor).
 9. Define attenuator.
 10. Define filter.
- Q.2** (a) Determine voltage, current and power relationship for three capacitors connected in series. **03**
- OR
- (a) Determine voltage, current and power relationship for three inductors connected in parallel. **03**
- (b) Explain Mesh analysis. **03**
- OR
- (b) Explain Node analysis. **03**

- (c) State Thevenin's Theorem. Only write necessary steps to calculate the load current in the circuit using Thevenin's Theorem. **04**
- OR
- (c) State Norton's Theorem. Only write necessary steps to calculate the load current in the circuit using Norton's Theorem. **04**
- (d) State and prove Maximum power transfer theorem. **04**
- OR
- (d) State and prove Super position theorem. **04**
- Q.3** (a) Prove that a series resonant circuit acts as a voltage amplifier at resonant frequency. **03**
- OR
- (a) Write difference of Q factor of coil and Q factor of capacitor. **03**
- (b) Find the Q factor of series circuit with resistance of $1\text{k}\Omega$, an inductor 100 mH and capacitor of $10\mu\text{F}$. **03**
- OR
- (b) Find the resonance frequency of series circuit with resistance of 10Ω , an inductor 0.2H and capacitor of $0.2\mu\text{F}$. **03**
- (c) Get the equation for resonance frequency for series R-L-C circuit. **04**
- OR
- (c) Get the equation for resonance frequency for parallel R-L-C circuit. **04**
- (d) Explain single tuned air core transformer. **04**
- OR
- (d) Explain iron core transformer. **04**
- Q.4** (a) Design symmetrical π attenuator with a load of $500\ \Omega$ and attenuation of 6dB . **03**
- OR
- (a) Design symmetrical T attenuator with a load of $300\ \Omega$ and attenuation of 20dB . **03**
- (b) Design a Constant K Type High Pass Filter with T section, if $f_c = 1.5\ \text{kHz}$ & $R_o = 400\ \text{ohms}$. **04**
- OR

- (b) Design m Derived Low Pass Filter with T section If $f_c = 1\text{kHz}$, $f_\infty = 1100\text{ Hz}$ & $R_o = 400\text{ Ohms}$ **04**
- (c) Classify the various types of equalizers. **07**
- Q.5** (a) Compare high pass, low pass, band pass and band stop filters. **04**
- (b) Explain how to convert T network into equivalent π network. **04**
- (c) Explain principle of Duality. **03**
- (d) Classify the various types of attenuators. **03**

પ્રશ્ન. ૧	દશમાંથી કોઈપણ સાતના જવાબ આપો.	૧૪
	૧. પેસિવ નેટવર્ક ને વ્યાખ્યાયીત કરો.	
	૨. નોન-લીનીયર નેટવર્ક ને વ્યાખ્યાયીત કરો.	
	૩. લૂમ્પડ નેટવર્ક ને વ્યાખ્યાયીત કરો.	
	૪. બાય લિટરલ નેટવર્ક ને વ્યાખ્યાયીત કરો.	
	૫. એ સીમેટ્રિકલ નેટવર્ક ને વ્યાખ્યાયીત કરો.	
	૬. કીર્યોફ ના કરંટ નીયમ ને સમજાવો	
	૭. બેંડવિથ ને વ્યાખ્યાયીત કરો.	
	૮. Q-ફેક્ટર ને વ્યાખ્યાયીત કરો.	
	૯. એટેન્યુટર ને વ્યાખ્યાયીત કરો.	
	૧૦ ફિલ્ટર ને વ્યાખ્યાયીત કરો.	
પ્રશ્ન. ૨	અ ત્રણ કેપેસીટર સીરીઝ મા કનેક્ટ કરેલા હોય તો વોલ્ટેજ, કરંટ અને પાવર શોધો.	૦૩
	અથવા	
	અ ત્રણ ઇન્ડક્ટર પેરેલલ મા કનેક્ટ કરેલા હોય તો વોલ્ટેજ, કરંટ અને પાવર શોધો.	૦૩
	બ મેશ એનાલીસીસ સમજાવો.	૦૩
	અથવા	
	બ નોડ એનાલીસીસ સમજાવો.	૦૩
	ક થેવેનિન થીયરમ લખો. થેવેનિન થીયરમ ની મદદ થી લોડ કરંટ શોધવા ના સ્ટેપ્સ લખો.	૦૪

અથવા

ક નોરટન થીયરમ લખો. નોરટન થીયરમ ની મદદ થી લોડ કરંટ શોધવા ના સ્ટેપ્સ લખો. 0૪

ડ મેક્સીમમ પાવર ટ્રાંસફર પ્રમેય લખો અને સાબીત કરો. 0૪

અથવા

ડ સુપર પોઝીસન પ્રમેય લખો અને સાબીત કરો. 0૪

પ્રશ્ન. ૩ અ સીરીઝ રીઝોનન્સ સર્કિટ રીઝોનન્સ ફ્રિકવંસી એ વોલ્ટેઝ એમ્પ્લિફાયર તરિકે કામ કરે તે સાબીત કરો. 0૩

અથવા

અ કોઇલ નો Q-ફેક્ટર અને કેપેસીટર નો Q-ફેક્ટર નો તફાવત લખો. 0૩

બ રેજિસ્ટંટ $1k\Omega$, ઇન્ડક્ટર 100 mH અને કેપેસીટર $10\mu\text{F}$ ના સીરીઝ જોડાણ માટે Q-ફેક્ટર શોધો. 0૩

અથવા

બ રેજિસ્ટંટ 10Ω , ઇન્ડક્ટર 0.2H અને કેપેસીટર $0.2\mu\text{F}$ ના સીરીઝ જોડાણ માટે રીઝોનન્સ ફ્રિકવંસી શોધો. 0૩

ક સીરીઝ RLC સર્કિટ માટે રીઝોનન્સ ફ્રિકવંસી શોધો. 0૪

અથવા

ક પેરેલલ RLC સર્કિટ માટે રીઝોનન્સ ફ્રિકવંસી શોધો. 0૪

ડ સીંગલ ટ્યુન એર કોર ટ્રાન્સફોર્મર સમજવો. 0૪

અથવા

ડ આયર્ન કોર ટ્રાન્સફોર્મર સમજવો. 0૪

પ્રશ્ન. ૪ અ $R_o = 500$ ઓહમ અને 6 dB એટેન્યુશન માટે સીમેટ્રીકલ π નેટવર્ક 03
એટેન્યુટર ની રચના કરો.

અથવા

અ $R_o = 300$ ઓહમ અને 20 dB એટેન્યુશન માટે સીમેટ્રીકલ T નેટવર્ક 03
એટેન્યુટર ની રચના કરો.

બ $f_c = 1.5$ kHz અને $R_o = 400$ ઓહમ માટે કોંસ્ટન્ટ K પ્રકાર ના હાઇ પાસ 04
ફીલ્ટર ના T સેકશન રચના કરો.

અથવા

બ $f_c = 1$ kHz, $f_\infty = 1100$ અને $R_o = 400$ ઓહમ માટે m પ્રકાર ના લો પાસ 04
ફીલ્ટર ના T સેકશન રચના કરો.

ક ઇકવલાઇઝર નુ વર્ગીકરણ આકૃતી સાથે સમજાવો. 09

પ્રશ્ન. ૫ અ હાઇ પાસ, લો પાસ, બેંડ પાસ અને બેંડ સ્ટોપ ફીલ્ટર સરખવો. 04

બ T-ટાઈપ નેટવર્ક માથી π - ટાઈપ ના નેટવર્ક મા રૂપાંતર માટે ના સમીકરણ 04
મેળવો.

ક ડ્યુઆલિટી નો પ્રીસીપલ સમજાવો. 03

ડ એટેન્યુટર નુ વર્ગીકરણ આકૃતી સાથે સમજાવો. 03
