

Seat No.: _____
No. _____

Enrolment

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING - SEMESTER-V • EXAMINATION – SUMMER • 2015

Subject Code: 350902

Date: 04-05-2015

Subject Name: Industrial Electronics

Time: 02:30 pm - 05:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Draw and explain the circuit of three phase full wave bridge type rectifier. Draw the waveforms and state the sequence of conduction of diode. **07**
- (b) Draw the control circuit using one UJT & two SCRs explain its working. **07**
- Q.2** (a) Explain the speed control of universal motor using TRIAC and DIAC. **07**
- (b) Explain the continuous & discontinuous conduction in motors operated from the controlled rectifier. **07**
- OR**
- (b) State methods of commutation and explain any one method with appropriate diagram. **07**
- Q.3** (a) Draw the circuit of half bridge and full bridge SCR inverters. Discuss their advantages and disadvantages. **07**
- (b) Explain construction, working and Turn on, Turn off process of MCT. **07**
- OR**
- Q.3** (a) Explain working of basic chopper circuit and explain the classification of chopper. **07**
- (b) Explain the use of chopper for the speed control of slip ring induction motor. **07**
- Q.4** (a) Explain with necessary sketches working principle of high frequency dielectric heating. Also list five applications and explain any one in brief. **07**
- (b) Discuss the difference between high frequency induction heating and dielectric heating. **07**
- OR**
- Q.4** (a) List out application of ultrasonic waves and explain how ultrasonic waves are detect cracks in the materials. **07**
- (b) State the advantages and disadvantage of induction heating. **07**
- Q.5** (a) Explain the sequence timer using IC555 and working with sketches. **07**
- (b) Write down types of resistance welding and explain any one in brief, state the advantages. **07**
- OR**
- Q.5** (a) Using mercury thermometer and photo device draw and explain circuit for the temperature control in the furnace. **07**
- (b) Explain the switch mode power supply with block diagram. **07**

5) Gv ! V YTML O[h O],J[J ATMLH 5TMSFZGF Z[IS8OFIZGM 5IZ5Y 07
 NMZLG[;DHFJM.T[GF VFp85]8 J[JOMD" NMZM.0FIM0GF
 JCGGM STMD ;DHFJM.
 A V[S UJT VG[A[SCR JF/M 5<; Sg8=M,GM p5IMU 07
 SZLG[[[[[[[[[Sg8=M, 5ZL5Y NMZM.

5) Gv Z V DIAC VG[TRIAC JF5ZL I]]]]GLJ;" , DM8ZGL UIT IGI\+LT 07
 SZJFGL SFI" 5NnlTVM ;DHFJM.
 A Sg8=M<0 Z[IS8OFIZYL RF,TL DM8ZDF\ ;TT VG[V;TT JCG 07
 ;DHFJM.

VYJF

A SMdI]8[XGL H]NL ZLTM H6FJM VG[SM. 56 V[S 5NnlT IMuI 07
 VFS'ITGL DNNYL ;DHFJM.

5) Gv # V CFO ATMLH VG[O], ATMLH SCR >GJ8"ZGL ;ZSL8 ¹MZM.T[GF 07
 ,FEF,FEFGL RRF" SZM.
 A MCT GM A\WFZ6,SFI"l;w3F\T,8G" VMO VG [8G" VMG 07
 ;DHFJM.

VYJF

5) Gv # V D}/E} }T RM5Z 5ZL5YG] SFI"" ;DHFJM. VG[RM5Z G] JUL"SZ6 07
 SZM.
 A ;,L5ZL\U >g0SXG DM8ZGF :5L0 Sg8=M, DF8[RM5ZGM p5IMU 07
 ;DHFJM.

5) Gv \$ V H~ZL VFS°IT ¹MZL CF.OTMLSJ;L >g0SXG CL8L\UGM SFI"v 07
 l;w3F\T ;DHFJM. >g0SXG CL8L\UGF 5F\R p5IMUMGL IF¹L
 VF5L SM. 56 V[S p5IMU 8\}SDF ;DHFJM.
 A CF.OTMLSJ;L >g0SXG CL8L\U VG[0FI .,[S8=LS CL8L\U 07
 JrR[GM TOFJ8 :5Q8 SZM.

VYJF

5) Gv \$ V V<8=F;MIGS J[JGF p5IMUMGL IF¹L AGFJM VG[V<8=F;MIGS 07
 D[8,DF\ TLZF0 XM3JFDF\ S[JL ZLT[J5ZFI K[T[;DHFJM.
 A >g0SXG CL8L\UGF ,FEF,FE ,BM. 07

5) Gv 5 V IC 555 GM p5IMU SZLG[;LSJg; 8F.DZGL ;ZSL8 NMZM VG[07
 ;DHFJM.
 A Z[hL:8g; J[<0L\UGF 5TMSFZM ,BM VG[SM. V[S G [8\}SDF 07
 ;DHFJM. Z[hL:8g; J[<0L\UGF OFINFVM H6FJM.

VYJF

5) Gv 5 V 5FZFG] pQ6TFDF5S VG[OM8M I0JF.; JF5ZL EoLGF TF5 07
 IGI\+6GM 5IZ5Y NMZL ;DHFJM.
 A B\0FS°ITGL DNNYL :JLr0 DM0 5FJZ ;%,FI ;DHFJM. 07
