

GUJARAT TECHNOLOGICAL UNIVERSITY

Diploma Engineering - SEMESTER-V • EXAMINATION – SUMMER • 2015

Subject Code: 351704

Date: 12-05-2015

Subject Name: Microprocessors, Interfacing and Applications

Time: 02:30 pm - 05:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) State True or False. **07**
(i) 8 Address and 8 data lines select 256 X 8 bit memory.
(ii) Decoder decodes n input lines to 2^{n-1} output line.
(iii) 8085 Microprocessor can address 0000H to FFFFH memory locations.
(iv) Memory map of 256 byte memory can be 8000H to 800FH.
(v) 8 bits of 8255 Port B can be used as individual bits.
(vi) 8255 has three 8 bits ports named A, B and C.
(vii) A is the only port used for all Modes 0,1 and 2 in 8255.
- (b) Compare memory mapped I/O interfacing with peripheral I/O. **07**
- Q.2** (a) Interface 8085 with 7 segment common anode LED display with device address FFD3H to display 80H using 3 to 8 decoder, latch & gates. **07**
(b) Explain control word format for 8255 mode 0. **07**
- OR
- (b) Write short note on 8255 BSR mode. **07**
- Q.3** (a) Write a program to generate square wave ($T_{on} = 10$ ms) using 1.5 MHz 8254. **07**
(b) Explain ICWs & OCWs formats of 8259 in brief. **07**
- OR
- Q.3** (a) Draw & explain block diagram of 8259. **07**
(b) Draw & explain block diagram of 8257. **07**
- Q.4** (a) Draw & explain block diagram of 8279. **07**
(b) Draw and explain functional block diagram of 8251. **07**
- OR
- Q.4** (a) Interface 8 bit ADC with 8085 using 8255, sample-hold & other circuits. **07**
(b) Interface 8 bit DAC with 8085 using 8255, OPAMP & other circuits. **07**
- Q.5** (a) List Microprocessor based applications. Explain microprocessor (μ P) based level monitoring system. **07**
(b) Explain microprocessor based temperature monitoring system. **07**
- OR
- Q.5** (a) Draw and explain block diagram of 8255. **07**
(b) Match the columns: **07**
- | | |
|------|---|
| 0801 | Programmable Peripheral Interface |
| 8255 | Programmable Interval Timer |
| 8259 | Programmable DMA Controller |
| 8254 | Programmable Keyboard/Display Interface |
| 8257 | Analog to Digital Converter |
| 8279 | USART |
| 8251 | Programmable Interrupt Controller |

ગુજરાતી

- પ્રશ્ન. ૧ અ ખરૂ અથવા ખોટું જણાવો. ૦૭
- (i) 8 એડ્રેસ અને 8 ડેટા લાઇનથી 256 X 8 બીટ સાઇઝની મેમરી પસંદ કરી શકાય.
- (ii) ડિકોડર n ઇનપુટ લાઇનને 2^{n-1} આઉટપુટ લાઇનોમાં ડિકોડ કરે છે.
- (iii) 8085 માઇક્રોપ્રોસેસર 0000H થી FFFFH સુધીનાં મેમરી સ્થાનો સંબોધી શકે.
- (iv) 256 બાઇટ મેમરીનો મેમરી મેપ 8000H થી 800FH સુધીનો હોય.
- (v) 8255નાં પોર્ટ B ની આઠેય બીટોનો વ્યક્તિગત બીટ તરીકે ઉપયોગ થઇ શકે.
- (vi) 8255 ને આઠ-આઠ બીટનાં A, B અને C એમ ત્રણ પોર્ટ હોય.
- (vii) ત્રણેય મોડ(0,1 & 2) માં ઉપયોગ થતો હોય તેવો 8255નો એકમાત્ર પોર્ટ A છે.
- બ મેમરી મેપ I/O ઇન્ટરફેસિંગની પેરિફરલ I/O સાથે સરખામણી કરો. ૦૭
- પ્રશ્ન. ૨ અ 8085 ને 3 to 8 ડિકોડર, લેચ અને ગેટ્સની મદદથી FFD3H એડ્રેસ ધરાવતા 7 ૦૭
- સેગમેન્ટ કોમન એનોડ LED ડિસ્પ્લે ઉપર 80H દર્શાવવા ઇન્ટરફેસ કરો.
- બ 8255 નાં મોડ 0 માટે કંટ્રોલ વર્ડ ફોર્મેટ લખીને સમજાવો. ૦૭
- અથવા
- બ 8255 નાં BSR મોડ ઉપર ટ્રેક નોંધ લખો. ૦૭
- પ્રશ્ન. ૩ અ 1.5 MHz 8254 દ્વારા 10 ms પહોળુ ચોરસ તરંગ બનાવતો પ્રોગ્રામ લખો. ૦૭
- બ 8259 નાં ICWs અને OCWs ફોર્મેટ લખીને ટ્રેકમાં સમજાવો. ૦૭
- અથવા
- પ્રશ્ન. ૩ અ 8259 નો બ્લોક ડાયગ્રામ દોરીને સમજાવો. ૦૭
- બ 8257 નો બ્લોક ડાયગ્રામ દોરીને સમજાવો. ૦૭
- પ્રશ્ન. ૪ અ 8279 નો બ્લોક ડાયગ્રામ દોરીને સમજાવો. ૦૭
- બ 8251 નો ઇંકશનલ બ્લોક ડાયગ્રામ દોરીને સમજાવો. ૦૭
- અથવા
- પ્રશ્ન. ૪ અ 8255, સેમ્પલ-હોલ્ડ અને અન્ય સર્કિટથી 8 બીટ ADCને 8085 સાથે જોડો. ૦૭
- બ 8255,ઓપરેશનલ એમ્પ્લીફાયર અને અન્યથી 8 બીટ DACને 8085 સાથે જોડો. ૦૭
- પ્રશ્ન. ૫ અ માઇક્રોપ્રોસેસર આધારિત ઉપયોગોની યાદી લખી સ્તર ચકાસણી પ્રણાલી સમજાવો. ૦૭
- બ માઇક્રોપ્રોસેસર આધારિત તાપમાન ચકાસણી પ્રણાલી સમજાવો. ૦૭
- અથવા
- પ્રશ્ન. ૫ અ 8255 નો બ્લોક ડાયગ્રામ દોરીને સમજાવો. ૦૭
- બ જોડકા જોડો. ૦૭
- | | |
|------|---|
| 0801 | પ્રોગ્રામેબલ પેરિફરલ ઇન્ટરફેસ |
| 8255 | પ્રોગ્રામેબલ ઇન્ટરવલ ટાઇમર |
| 8259 | પ્રોગ્રામેબલ DMA કન્ટ્રોલર |
| 8254 | પ્રોગ્રામેબલ કીબોર્ડ/ ડિસ્પ્લે ઇન્ટરફેસ |
| 8257 | એનલોગ ટુ ડિઝીટલ કન્વર્ટર |
| 8279 | યુઝર્ટ |
| 8251 | પ્રોગ્રામેબલ ઇન્ટરપ્ટ કન્ટ્રોલર |
