

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Semester –II Remedial Examination December - 2010****Subject Code: 320017****Subject Name: E.D.C.-I****Date: 20 /12 /2010****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instruction:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version Authentic

- Q.1** (a) With the help of energy band diagram explain the insulator, conductor and semi conductor. **06**
 (b) Explain the difference between the Intrinsic and the extrinsic semiconductor. **04**
 (c) Give the methods of fabrication of PN junction diode & explain any one method. **04**
- Q.2** (a) Derive the equation for I_{dc} and I_{RMS} for a full wave rectifier and from this obtain the ripple factor. **07**
 (b) Explain clamping circuits with waveform. **07**
- OR**
- (b) (i) Draw and explain characteristics of LDR **07**
 (ii) State advantages and disadvantages of photo transistor compared to Photo diode.
- Q.3** (a) Explain the working of NPN transistor. **05**
 (b) Define α and β of transistor and obtain relation between them. **04**
 (c) Compare CE, CB and CC amplifier. **05**
- OR**
- Q.3** (a) Determine A_v , A_i , A_P , R_O and R_i using CE amplifier. Explain DC load line & operating point. **05**
 (b) Explain the working of common base amplifier. **04**
 (c) Draw the circuit of Darlington amplifier and explain it's working. **05**
- Q.4** (a) Draw the circuit of two stages transformer coupled amplifier. State it's advantages and disadvantages. **07**
 (b) State reasons for thermal instability. Explain potential divider method of biasing. **07**
- OR**
- Q.4** (a) Draw & explain circuit of directly coupled two stage amplifier & state its advantage & disadvantage. **07**
 (b) Explain H parameter of CE configuration. Find out voltage gain, Current gain & input impedance of CE amplifier using approximate model formulas if $h_{ie}=1k\Omega$, $h_{fe}=100$, $h_{re}=5*10^{-4}$, $h_{oe}=10^{-6}s$, $R_c=4.7k\Omega$. **07**
- Q.5** (a) Derive hybrid parameters for transistor amplifier considering transformer as a four terminal network. **07**
 (b) (i) What is heat sink? Explain need of heat sink? **03**
 (ii) Explain (i) zener break down (ii) Avalanche break down. **04**
- OR**
- Q.5** (a) Draw & Explain Block dia of SMPS **06**
 (b) Write a short note on UPS **05**
 (c) Draw voltage regulator using three terminal IC 7805. **03**

Q.1	અ	કન્ડક્ટર, સેમી કન્ડક્ટર અને ઈન્સ્યુલેટર માટે એનર્જી લેવલ ડાયાગ્રામ સમજાવો.	06
	બ	ઈન્ટ્રેન્સીક અને એક્સઈન્ટ્રેન્સીક સેમી કન્ડક્ટર વચ્ચેનો તફાવત સમજાવો.	04
	ક	પી.એન જકંશન બનાવવાની પદ્ધતિઓ જણાવો અને કોઈપણ એક પદ્ધતિ સમજાવો.	04
Q.2	અ	ફૂલ વેવ રેક્ટીફાયર માટે Idc અને IRMS નું સૂત્ર તારવો અને તેમાથી રીપલ ફેક્ટરનું સૂત્ર મેળવો.	07
	બ	પરીપથેની આકૃતિ અને વેવફોર્મ સહિત કલેમર્પીંગ પરીપથ સમજાવો.	07
		<u>અથવા</u>	
	અ	(1) LDR ની લાક્ષણિકતાઓ આકૃતિ સહિત સમજાવો.	07
	બ	(2) ફોટો ડાયોડની સરખામણીએ ફોટો ટ્રાન્સીસ્ટરના ફાયદા અને ગેરફાયદા જણાવો.	
Q.3	અ	એનપીએન ટ્રાન્સીસ્ટરની કાર્યપદ્ધતિ જણાવો.	05
	બ	α (આલ્ફા) અને β (બીટા)ની ટ્રાન્સીસ્ટર માટે વ્યાખ્યા આપો. બંને વચ્ચેના સબંધોનું સમીકરણ તારવો.	04
	ક	સીઈ, સીબી અને સીસી એમ્પ્લીફાયર સરખામણી કરો.	05
		<u>અથવા</u>	
Q.3	અ	સીઈ એમ્પ્લીફાયર માટે Av, Ai, AP, RO અને Riના સૂત્રો તારવો. અને ડીસી લોડલાઈન અને ઓપરેટીંગ પોઈન્ટ સમજાવો.	05
	બ	કોમન બેઝ એમ્પ્લીફાયર કાર્યપદ્ધતિ સમજાવો.	04
	ક	યોગ્ય પરીપથ દોરી ડાર્લિંગટન એમ્પ્લીફાયર કાર્યપદ્ધતિ સમજાવો	05
Q.4	અ	ટુ સ્ટેજ ટ્રાન્સફોર્મર કપલ્ડ એમ્પ્લીફાયરનો યોગ્ય પરીપથ દોરો. અને તેના ફાયદા અને ગેરફાયદા જણાવો.	07
	બ	થર્મલ અસ્થિરતા માટેના કારણો આપો. અને બાયસીંગની પોટેન્સીયલ ડીવાયડરની પદ્ધતિ સમજાવો.	07
		<u>અથવા</u>	
Q.4	અ	યોગ્ય પરીપથ દોરી ટુ સ્ટેજ ડાયરેક્ટ કપલ્ડ એમ્પ્લીફાયર સમજાવો. અને તેના ફાયદા અને ગેરફાયદા જણાવો.	07
	બ	સીઈ એમ્પ્લીફાયરના બંધારણ માટે એચ પેરામીટર તારવો અને સીઈ એમ્પ્લીફાયર માટે વોલ્ટેજ ગેઈન , કરંટ ગેઈન અને ઈનપુટ ઈમ્પીડન્સ શોધો. જો $h_{ie}=1k\Omega$, $h_{fe}=100$, $h_{re}=5*10^{-4}$, $h_{oe}=10^{-6}s$, $R_c= 4.7k\Omega$.	07
Q.5	અ	ટ્રાન્સીસ્ટરને ચાર ટર્મીનલનો નેટવર્ક ધારીને ટર્મીનલ એમ્પ્લીફાયરના હાઈબ્રીડ પેરામીટર તારવો.	07
	બ	(1) હીટસીંક શુ છે? અને તેની જરૂરીયાત સમજાવો.	03
		(2) (i) ઝેનર બ્રેકડાઉન (ii) એવલાન્ચ બ્રેકડાઉન	04
		<u>અથવા</u>	
	અ	યોગ્ય બ્લોક ડાયાગ્રામ દ્વારા SMPS નું કાર્ય સમજાવો.	06
	બ	UPS નું વિશે ટૂંકમાં લખો.	05
	ક	ત્રણ ટર્મીનલ આઈસી ૭૮૦૫ નો ઉપયોગ કરી વોલ્ટેજ રેગ્યુલેટ દોરો.	03
