

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering Semester –I/II Examination Jan. 2012

Subject code: 320017

Date: 11/01/2012

Subject Name: Electronic Devices and Circuit-I

Time: 10.30 am – 01.00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered Authentic.

Q.1	(a) Draw the characteristics of PN junction diode and explain it in detail.	07
	(b) Derive an expression for the ripple factor of half-wave rectifier.	07
Q.2	(a) Explain how a transistor can act as an amplifier	07
	(b) With the help of d.c.load line analyze the common emitter amplifier.	07
	OR	
	(b) Explain Darlington pair in detail.	07
Q.3	(a) Explain stability factor and reasons for thermal instability	07
	(b) Explain potential divider biasing method for stabilization	07
	OR	
Q.3	(a) Draw the circuit of two stage RC coupled amplifier and explain its frequency response.	07
	(b) Explain high frequency response of a pulse to CE amplifier.	07
Q.4	(a) Derive h-parameters for CE amplifier.	07
	(b) State and explain the advantages of h- parameters.	07
	OR	
Q. 4	(a) What is regulated power supply? Draw it's block diagram and explain the function of each block in detail.	07
	(b) Draw circuit of shunt regulator using transistor and explain it's working in detail.	07
Q.5	Write short notes on	
	(a) Varactor diode	07
	(b) Light emitting diode	07
	OR	
Q.5	Write short notes on	
	(a) Stabilizer	07
	(b) Common collector amplifier	07

પ્ર.૧	(અ) પી.એન.જંકસન ડાયોડની લાક્ષણીકતાઓ દોરો. અને વિગતવાર સમજાવો..	07
	(બ) હાફ વેવ રેક્ટીફિયરના રીપલ ફેક્ટરના સમીકરણો મેળવો.	07
પ્ર.૨	(અ) ટ્રાંજુસ્ટર એપલીફાયર તરીકે કેવી રીતે કામ કરે છે તે સમજાવો.	07
	(બ) કોમન એમીટર એપલીફાયરનું પુથક્કરણ ડી.સી. લોડ લાઇનની મદદથી કરો.	07
અથવા		
	(બ) ડાલીંગાટન પેર વિગતવાર સમજાવો..	07
પ્ર.૩	(અ) સ્ટેબીલીટી ફેક્ટર અને થર્મલ ઇન્સ્ટેબીલીટીના કારણો સમજાવો..	07
	(બ) સ્ટેબીલાઇજેસન માટે પોટેન્શીયલ ડીવાઇડર બાયાસિંગ રીત સમજાવો.	07
અથવા		
પ્ર.૩	(અ) ટુ સ્ટેજ આર.સી. કપલ એપલીફાયરની સરકીટ દોરો અને તેનો ફીકવંસી રીસ્પોંસ સમજાવો	07
	(બ) સી.ઇ. એપલીફાયરનો હાઇ ફીકવંસી પલ્સ રીસ્પોંસ સમજાવો	07
પ્ર.૪	(અ) સી.ઇ. એપલીફાયર માટે એચ પેરામીટર તારવો.	07
	(બ) એચ. પેરામીટરના ફાયદા લખો અને સમજાવો.	07
અથવા		
પ્ર.૪	(અ) રેગ્યુલેટેડ પાવર સપ્લાય શું છે? તેનો બ્લોક ડાયાગ્રામ દોરો અને દરેક બ્લોકનું કાર્ય વિગતવાર સમજાવો..	07
	(બ) ટ્રાંજુસ્ટરનો ઉપયોગ કરીને શન્ટ રેગ્યુલેટરની સરકીટ દોરો તેનું કાર્ય વિગતવાર સમજાવો..	07
પ્ર.૫	નોંધ લખો	
	(અ) વેરેક્ટર ડાયોડ	07
	(બ) લાઇટ એમીટીંગ ડાયોડ	07
અથવા		
પ્ર.૫	નોંધ લખો	
	(અ) સ્ટેબીલાઇજર	07
	(બ) કોમન કલેક્ટર એપલીફાયર	07
