

GUJARAT TECHNOLOGICAL UNIVERSITY
Diploma Engineering Semester –III Examination Dec. 2011

Subject code: 331102

Date: 23/12/2011

Subject Name: Digital Electronics

Time: 10.30 am – 01.00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered Authentic.

- Q.1** (a) Convert following Binary numbers into Hex and Decimal numbers **07**
 (i) 101010.10 (ii) 1101
- (b) For i/p A, B and o/p Y, Draw symbols of AND,NAND,OR,NOR,Ex-OR **07**
 ,Ex-NOR and NOT logic gates and write truth tables for each.
- Q.2**
- (a) State and prove Demorgan's theorem. **07**
 (b) Using NAND gates, realize NOR and EX-OR gates **07**
 OR
- (b) What is Universal gate? Realize OR, AND gates using universal gates. **07**
- Q.3**
- (a) Calculate following and find the answer: **07**
 (i) $(1D)_{16} + (111)_2 = (\dots\dots)_{10}$
 (ii) $(256)_{10} = (\dots\dots)_{16} = (\dots\dots)_8 = (\dots\dots)_2$
- (b) Simplify following using Boolean algebra **07**
 (i) $Y = A'BC + ABC + BC'$ (ii) $Y = AB'C + ABC + A'C$
 OR
- Q.3** (a) Compare combinational and sequential circuits. **07**
 (b) Explain Edge triggered J K Flipflop using truth table and its figure. **07**
- Q.4**
- (a) Write truth table of full adder and draw its logic circuit. **07**
 (b) Using logic gates, draw and explain circuit of 3 X 8 decoder. **07**
 OR
- Q. 4** (a) Draw Karnaugh maps for following three variables X,Y,Z and simplify it **07**
 :
 (i) $F = \sum m(0,1,4,5,6)$ (ii) $F = \sum m(0,1,2,4)$
- (b) Using logic gates, draw and explain circuit of 4 X 1 multiplexer. **07**
- Q.5**
- (a) Write full forms of RTL, DTL,TTL, MOS, CMOS logic families and **07**
 compare these logic families.
- (b) Draw and explain in brief : D flipflop and T flipflop **07**
 OR
- Q.5** (a) Draw and explain 4 bit binary up counter. **07**
 (b) Using block diagram, explain successive approximation ADC **07**

- પ્ર.1
- (a) નીચેના બાયનરી નંબરોને હેક્ષ તથા ડેસીમલ નંબરોમાં બદલો. 07
 (i) 101010.10 (ii) 1101
- (b) i/p A, B અને o/p Y માટે, AND, NAND, OR, NOR, Ex-OR, Ex-NOR અને NOT ગેટના સિમ્બોલ દોરો અને દરેકના ટ્રુથ ટેબલ લખો. 07
- પ્ર.2
- (a) ડી મોર્ગન થીયરમ લખો અને સાબિત કરો. 07
- (b) NAND ગેટના ઉપયોગથી NOR અને EX-OR ગેટ બનાવો. 07
 અથવા
- (b) યુનિવર્સલ ગેટ એટલે શું? યુનિવર્સલ ગેટના ઉપયોગથી OR અને AND ગેટ બનાવો. 07
- પ્ર.3
- (a) નીચેનાની ગણતરી કરી જવાબ મેળવો: 07
 (i) $(1D)_{16} + (111)_2 = (\dots\dots)_{10}$
 (ii) $(256)_{10} = (\dots\dots)_{16} = (\dots\dots)_8 = (\dots\dots)_2$
- (b) બુલીયન એલ્જીબ્રાની મદદથી નીચેનાનું સાદું રૂપ આપો. 07
 (i) $Y = A'BC + ABC + BC'$ (ii) $Y = AB'C + ABC + A'C$
 અથવા
- પ્ર.3 (a) કોમ્પીનેશનલ અને સીક્વન્શલ સર્કીટની સરખામણી કરો. 07
- (b) એઇજ ટ્રીગ્ગર્ડ JK ફ્લોપ ફ્લોપ તેના ટ્રુથ ટેબલ તથા આકૃતિની મદદથી સમજાવો. 07
- પ્ર.4
- (a) કુલ એડરનું ટ્રુથ ટેબલ દોરો અને એની સર્કીટ દોરી સમજાવો. 07
- (b) લોજીક ગેટની મદદથી 3 X 8 ડીકોડર બનાવો અને સમજાવો. 07
 અથવા
- પ્ર. 4 (a) નીચેના ત્રણ વેરીએબલ માટે કાર્નોપ મેપ દોરો અને સાદું રૂપ આપો : 07
 (i) $F = \sum m(0,1,4,5,6)$ (ii) $F = \sum m(0,1,2,4)$
- (b) લોજીક ગેટના ઉપયોગથી 4 X 1 મલ્ટીપ્લેક્સર દોરો અને સમજાવો. 07
- પ્ર.5
- (a) RTL, DTL, TTL, MOS, CMOS લોજીક ફેમીલીના કુલ ફોર્મ લખો અને તેની સરખામણી કરો. 07
- (b) આની વિશે ટૂંક નોંધ લખો: (i) D ફ્લોપ ફ્લોપ (ii) T ફ્લોપ ફ્લોપ 07
 અથવા
- પ્ર.5 (a) 4 બીટ બાયનરી અપ કાઉન્ટર દોરો અને સમજાવો. 07
- (b) બ્લોક ડાયાગ્રામની મદદથી સક્સેસીવ એપ્રોક્ષીમેશન ટાઇપ ADC સમજાવો. 07
