

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering Semester –IV Examination Dec. - 2011****Subject code: 342401****Date: 07/12/2011****Subject Name: Elements of Power Electronics****Time: 10.30 am – 1.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered Authentic.

- Q.1** (a) Give the difference between Thyristor and Transistor. **07**
 (b) List the different modes of operation of a thyristor and with the help of its static V-I characteristics explain “reverse blocking mode” of operation in brief. **07**

- Q.2** (a) List various triggering methods of SCR and discuss GATE triggering method in detail. **07**
 (b) Draw and explain the equivalent circuit and V-I Characteristics of the UJT in detail. **07**

OR

- (b) Describe the working of UJT relaxation oscillator with circuit and waveforms. **07**
- Q.3** (a) The latching current (50mA) of a thyristor circuit connected in series with voltage source of $V_s=100V$, Resistor $R=20\Omega$, Inductor $L=0.5$ Henry is 50mA. The duration of firing pulse is $50\mu s$. Will the thyristor get fired? **07**

- (b) What do you mean by commutation of SCR? Discuss class-B commutation in detail. **07**

OR

- Q.3** (a) What are the basic conditions to turn-off a conducting SCR? Discuss class-C commutation in detail. **07**
 (b) For a series connected Diode, DC Voltage source V_s with LC-load circuit, **07**

derive $i(t)=V_s\sqrt{\frac{C}{L}}\sin\omega t$ and $V(t)=V_s(1-\cos[\omega t])$. Also support the above equation with waveforms.

- Q.4** (a) Explain series operation of three SCRs connected in series. **07**
 (b) Derive $V_o = \frac{V_m}{2\pi}(1 + \cos\alpha)$ for a 1-phase half controlled rectifier with R-Load. Also draw related waveforms. **07**

OR

- Q.4** (a) Explain parallel operation of three SCRs connected in parallel. **07**
 (b) Draw circuit diagram, waveforms for a 1-phase full controlled rectifier with R-Load. **07**

- Q.5** (a) Explain Gate turn off thyristor (GTO) in detail. **07**
 (b) Explain power MOSFET in detail **07**

OR

- Q.5** (a) Draw and explain the 1- phase ac controller using DIAC-TRIAC. **07**
 (b) What do you mean by power electronics? Give brief introduction about thyristor family and make a list of it's applications in power electronics. **07**

પ્રશ્ન-૧	અ	Thyristor અને Transistor નો તફાવત આપો.	07
	બ	Thyristor ના જુદા-જુદા મોડ ના ઓપરેશન નિ યાદી બનાવો અને સ્ટેટિક V-I કેરેક્ટરિસ્ટીક નિ મદદ થિ “રીવર્સ બ્લોકિંગ મોડ” નુ ટુક મા વર્ણન કરો. .	07
પ્રશ્ન-૨	અ	Thyristor ની જુદી-જુદી ટ્રિગરિંગ પદ્ધતી નિ યાદી બનાવો અને ગેટ ટ્રિગરિંગ પદ્ધતી ટુક મા નુ વર્ણન કરો.	07
	બ	UJT ની equivalent (સમાંતર) સર્કિટ અને સ્ટેટિક V-I કેરેક્ટરિસ્ટ ઈરો અને તેનુ વર્ણન કરો.	07
		અથવા	
	બ	UJT Relaxation Oscillator નુ સર્કિટ અને વેવફોર્મ સાથે વર્ણન કરો..	07
પ્રશ્ન-૩	અ	એક સીરીજ સર્કિટ મા સોર્સ વોલ્ટેજ $V_s = 100\text{Volt}$ ની સીરીજ મા Resistor $R=20\Omega$, Inductor $L=0.5\text{ Henry}$ જોડેલ છે.જ્યારે Thyristor નો લેચિંગ કરંટ 50mA અને ફાયરીંગ પલ્સ નો સમય $50\ \mu\text{s}$ છે.તો શુ Thyristor ચાલુ (on) થશે?	07
	બ	SCR નુ કોમ્યુટેશન એટલે શુ? Class-B કોમ્યુટેશન નિ વિગતે ચર્ચા કરો.	07
પ્રશ્ન-૩		અથવા	
	અ	કન્ડક્ટિંગ SCR ને ટર્ન ઓફ (બંધ) કરવાની પાયા નિ શરતો કઈ? Class-C કોમ્યુટેશન નિ વિગતે ચર્ચા કરો.	07
	બ	સીરીજ કનેક્ટેડ સર્કિટ મા જોડેલ ડાયોડ,વોલ્ટેજ સોર્સ અને RL-લોડ નિ સર્કિટ માટે સાબીત કરો કે $i(t)=V_s\sqrt{\frac{C}{L}}\sin\omega t$ અને $V(t)=V_s(1-\cos[\omega t])$.ઉપર ના સુત્રો ને વેવ ફોર્મ થિ સમજાવો.	07
પ્રશ્ન-૪	અ	સીરીજ મા જોડેલ ત્રણ SCR ની સર્કિટ(series connection of SCR) નુ વર્ણન કરો..	07
	બ	1-ફેજ હાફ કંટ્રોલ્ડ રેક્ટિફાયર મા R- લોડ માટે $V_o = \frac{V_m}{2\pi}(1 + \cos\alpha)$ સુત્ર તારવો અને જરૂરી વેવફોર્મ ઈરો.	07
પ્રશ્ન-૪		અથવા	
	અ	પેરેલલ મા જોડેલ ત્રણ SCR ની સર્કિટ(parallel connection of SCR) નુ વર્ણન કરો.	07
	બ	1-ફેજ ફુલ કંટ્રોલ્ડ રેક્ટિફાયર મા R- લોડ માટે સર્કિટ ડયાગ્રામ, વેવફોર્મ ઈરો.	07
પ્રશ્ન-૫	અ	ગેટ ટર્ન ઓફ થાયરીસ્ટર(GTO) નુ સમ્પુર્ણ વર્ણન કરો.	07
	બ	Power MOSFET નુ સમ્પુર્ણ વર્ણન કરો.	07
પ્રશ્ન-૫		અથવા	
	અ	DIAC-TRIAC દ્વારા સિંગલ ફેજ AC કંટ્રોલર ની આકૃતી ઈરો અને તેનુ વર્ણન કરો.	07
	બ	પાવર ઇલેક્ટ્રોનિક્સ વિશે તમે શુ સમજો છો? થાયરીસ્ટર નિ ફેમિલિ વિશે ટુક મા લખો અને પાવર ઇલેક્ટ્રોનિક્સ માટે તેની ઉપયોગીતા વિશે યાદી બનાવો.	07
