

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGG.- SEMESTER-III EXAMINATION – WINTER 2012

Subject code: 331102

Date: 03/01/2013

Subject Name:

Time: 2:30 pm – 5:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- Q.1** (a) Do following conversions:
- (1) $10001100_2 = \text{_____}_{16} = \text{_____}_8$ **04**
- (2) $23.45_{10} = \text{_____}_2$ **03**
- (b) Perform following:
- (1) $111 \times 101 = \text{_____}_2$; $11011 \div 100 = \text{_____}_2$ **04**
- (2) $1111 - 1011 = \text{_____}_2$; $100011 - 111010 = \text{_____}_2$ **03**
- Q.2** (a) Draw the circuit of TTL NAND gate and explain its working. **07**
- (b) State De-Morgan's theorems and prove it. **07**
- OR**
- (b) Prove (i) $(ABC)' = A' + B' + C'$ (ii) $(A+B+C)' = A'B'C'$ **07**
- Q.3** (a) Draw the circuit diagram of CMOS and explain its function. **07**
- (b) State universal gates and realize Ex-OR gate using NAND gate. **07**
- OR**
- Q.3** (a) Define these terms: (i) Fan-in (ii) Fan-out (iii) Noise Immunity **07**
- (iv) Propagation Delay (v) Saturation Delay (vi) t_{hold} (vii) t_{setup}
- (b) Simplify following using Boolean algebra and draw the logic circuit **07**
- $Y = ABC + AB'C + ABC'$
- Q.4** (a) Write truth-table of full-adder and realize circuit using two half-adders. **07**
- (b) Using logic gates draw and explain circuit of multiplexer. **07**
- OR**
- Q.4** (a) Draw Karnaugh map: a truth table has output 1s for these inputs **07**
- ABCD=0000; 0010; 1000 and 1010.
- (b) Using logic gates draw and explain 1-of-16 decoder. **07**
- Q.5** (a) Draw and explain 4-bit binary ripple counter (serial counter). **07**
- (b) Write short notes on: (i) SR Flip-flop (ii) JK M/S Flip-flop. **07**
- OR**
- Q.5** (a) (i) Draw and explain R-2R ladder D/A converter. **07**
- (ii) Compare static and dynamic RAM.
- (b) Using block diagram, explain successive approximation ADC. **07**

પ્રશ્ન-૧	અ	નીચે મુજબ ના રૂપાંતરણો કરો (૧) $10001100_2 = \text{_____}_{16} = \text{_____}_8$ (૨) $23.84_{10} = \text{_____}_2$	07
	બ	આની ગણતરી કરો (૧) $111 \times 101 = \text{_____}_2$; $11011 \div 100 = \text{_____}_2$ (૨) $1111 - 1011 = \text{_____}_2$; $100011 - 111010 = \text{_____}_2$	07
પ્રશ્ન-૨	અ	TTL NAND ગેટ ની સર્કિટ દોરો અને તેનું કાર્ય સમજાવો.	07
	બ	ડી-મોર્ગનના થીયરમ લખો અને સાબિત કરો. અથવા	07
	બ	સાબિત કરો: (૧) $(ABC)' = A' + B' + C'$ (૨) $(A+B+C)' = A'B'C'$	07
પ્રશ્ન-૩	અ	CMOS ની સર્કિટ દોરો અને તેનું કાર્ય સમજાવો.	07
	બ	યુનિવર્સલ ગેટ્સ ના નામ લખો અને NAND ગેટ ના ઉપયોગથી Ex-OR ગેટ બનાવો. અથવા	07
પ્રશ્ન-૩	અ	આની વ્યાખ્યા આપો: (૧) ફેન ઇન (૨) ફેન આઉટ (૩) નોઈઝ ઇમ્યુનિટી (૪) પ્રપોગેશન ડીલે (૫) સેચ્યુરેશન ડીલે (૬) t_{hold} (૭) t_{setup}	07
	બ	બુલીયન એલ્જીબ્રાની મદદથી નીચેનાનું સાદું રૂપ આપો અને તેની લોજિક સર્કિટ દોરો $Y = ABC + AB'C + ABC'$	07
પ્રશ્ન-૪	અ	કુલ એડરનું ટ્રુથ ટેબલ દોરો અને હાફ એડરની મદદથી એની સર્કિટ દોરો.	07
	બ	લોજિક ગેટનાં ઉપયોગથી મલ્ટીપ્લેક્સરની સર્કિટ દોરો અને સમજાવો. અથવા	07
પ્રશ્ન-૪	અ	એક ટ્રુથ ટેબલ કે જેનું આઉટપુટ ૧ છે ઇનપુટ ABCD = 0000; 0010; 1000; 1010 માટે, તેના માટે કાર્નોહ મેપ દોરો.	07
	બ	લોજિક ગેટનાં ઉપયોગથી 1×15 ડીકોડર બનાવો અને સમજાવો.	07
પ્રશ્ન-૫	અ	૪-બીટ બાયનરી રીપલ કાઉન્ટર દોરો અને સમજાવો.	07
	બ	ટુંક નોંધ લખો: (૧) SR ફ્લોપ ફ્લોપ (૨) JK M/S ફ્લોપ ફ્લોપ. અથવા	07
પ્રશ્ન-૫	અ	(૧) R-2R લેડર D/A કન્વર્ટર દોરો અને સમજાવો. (૨) સ્ટેટીક અને ડાયનામિક RAM ની સરખામણી કરો.	07
	બ	બ્લોક ડાયાગ્રામની મદદથી સક્સેસીવ એપ્રોક્સીમેશન ADC સમજાવો.	07
