

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma Engineering - SEMESTER-III • EXAMINATION – WINTER 2013****Subject Code: 331102****Date: 30-11-2013****Subject Name: Digital Electronics****Time: 02:30 pm - 05:00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Each question carry equal marks (14 marks)

- Q.1** (a) Answer the following: **04**
 (i) Explain De-Morgan's theorems. **03**
 (ii) Explain binary to gray code converter. **07**
 (b) Convert the decimal number to binary, octal and hexadecimal. **07**
 (i) 250 (ii) 422.48
- Q.2** (a) Discuss NAND, NOR, EX-OR, EX-NOR gates with the help of symbols, operation and truth table. **07**
 (b) Perform (i) $(111011.11)_2 = (\quad)_8 = (\quad)_{10}$. **04**
 (ii) $(1E)_{16} + (10)_8 + (111)_2 = (\quad)_{10}$ **03**
- OR
- (b) Explain Combinational and Sequential circuit & compare it. **07**
- Q.3** (a) Draw the logic diagram of full adder using two half adder and an OR gate & explain it with truth table. **07**
 (b) Write short note on: J K Flip flop. **07**
- OR
- Q.3** (a) What is Multiplexer and Demultiplexer ? Discuss its application. **07**
 (b) Draw and explain 4 bit synchronous Up/Down Counter. **07**
- Q.4** (a) Obtain the simplified expression of following function with K-map . **07**
 $f(A,B,C,D) = \sum_m(1,2,7,13) + d(3,5,9,10)$
 (b) Give classification of memory and compare static & dynamic RAM. **07**
- OR
- Q.4** (a) Explain Successive approximation method for Analog to Digital conversion. **07**
 (b) List the advantages and disadvantages of CMOS logic family. Draw & explain the circuit of 2 input CMOS NOR gate. **07**
- Q.5** (a) Discuss 3 x 8 Decoder and 8 x 3 Encoder circuit. **07**
 (b) Explain types of Registers. Draw circuit diagram of serial input serial output register to shift 1101 input data with waveform. **07**
- OR
- Q.5** (a) Define : (i) Fan-in (ii) Fan-out (iii) Noise margin. (iv) Propagation delay. **07**
 (b) Explain the circuit diagram of BCD adder. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ નિચેના જવાબ આપો: ૦૪
- (i) ડી-મોરગન ના પ્રમેય સમજાવો. ૦૩
- (ii) બાયનરી થી ગ્રે કોડ કન્વર્ઝન સમજાવો.
- બ ડેસિમલ માંથી બાયનરી, ઓક્ટલ, હેક્ઝા ડેસિમલ નંબર માં તબ્દીલ કરો. ૦૭
- (i) 250 (ii) 422.48
- પ્રશ્ન. ૨ અ NAND, NOR, EX-OR, EX-NOR ગેટ ના સિમ્બોલ, ઓપ્રેશન અને ત્રુથ ટેબલ ૦૭
- ની મદ્દ થી વર્ણવો.
- બ તબ્દીલ કરો (i) $(111011.11)_2 = (\quad)_8 = (\quad)_{10}$. ૦૪
- (ii) $(1E)_{16} + (10)_8 + (111)_2 = (\quad)_{10}$ ૦૩
- અથવા
- બ કોમ્પીનેશનલ અને સીક્યુવેંશીયલ સર્કીટ સમજાવો અને તેના તફાવત વર્ણવો. ૦૭
- પ્રશ્ન. ૩ અ બે હાફ એડર અને OR ગેટ ની મદ્દ થી ફુલ એડર ની આકૃતિ દોરી ત્રુથ ટેબલ ૦૭
- સાથે સમજાવો.
- બ ટૂક નોંધ લખો : J K Flip flop. અથવા ૦૭
- પ્રશ્ન. ૩ અ મલ્ટીપ્લેક્સર અને ડી મલ્ટીપ્લેક્સર શું છે ? તેના વિવિધ ઉપયોગ વર્ણવો. ૦૭
- બ 4 bit સીક્યુવેંશીયલ Up/Down કાઉંટર ની આકૃતિ દોરી સમજાવો. ૦૭
- પ્રશ્ન. ૪ અ K-map ની મદ્દ થી સિમ્પલીફાઇડ સમીકરણ સોધો. ૦૭
- $f(A,B,C,D) = \sum_m(1,2,7,13) + d(3,5,9,10)$
- બ મેમરી ના વિવિધ પ્રકાર વર્ણવો. સ્ટેટીક અને ડાઇનમીક RAM તફાવત વર્ણવો. ૦૭
- અથવા
- પ્રશ્ન. ૪ અ એનાલોગ થી ડીઝીટલ કન્વર્ઝન ની સક્સેસીવ એપ્રોક્સીમેશન પદ્ધતી ૦૭
- સમજાવો.
- બ CMOS લોજીક ફેમીલીના ફાયદાઓ વર્ણવો. 2 input CMOS NOR ગેટ ની ૦૭
- આકૃતિ દોરી સમજાવો.
- પ્રશ્ન. ૫ અ 3 x 8 ડીકોડર અને 8 x 3 એનકોડર ની આકૃતિ દોરી સમજાવો. ૦૭
- બ રેજીસ્ટર ના વિવિધ પ્રકાર સમજાવો. સિરીયલ ઇનપુટ સિરીયલ આઉટપુટ સિફ્ટ ૦૭
- રેજીસ્ટર માં ૧૧૦૧ ડેટાને સિફ્ટ કરવાની પદ્ધતી વેવફોર્મ સાથે સમજાવો.
- અથવા
- પ્રશ્ન. ૫ અ વ્યાખ્યા આપો : (i) ફેન-ઇન (ii) ફેન-આઉટ (iii) નોઇસ મારજીન (iv) પ્રોપગેશન ૦૭
- ડીલે.
- બ BCD એડર ની આકૃતિ દોરી સમજાવો. ૦૭
