

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
DIPLOMA ENGINEERING - SEMESTER-VI • EXAMINATION – WINTER • 2014

Subject Code: 361102

Date: 28-11-2014

Subject Name: VLSI Technology

Time: 02:30 pm - 05:00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is considered to be Authentic.

- Q.1** (a) Explain VLSI design flow using Y- Chart. **07**
(b) Explain criteria for Design quality improvement. **07**
- Q.2** (a) Write short note on FPGA. **07**
(b) Explain NMOS inverter with Resistive Load. **07**
OR
(b) Explain Depletion load NMOS inverter. **07**
- Q.3** (a) Draw and explain CMOS NOR2 gate. **07**
(b) Explain the operation of MOSFET transistor. **07**
OR
- Q.3** (a) Draw and explain CMOS NAND2 gate. **07**
(b) Draw and explain Energy band diagram for MOS structure. **07**
- Q.4** (a) Draw & Explain CMOS SR latch using NAND2 gate. **07**
(b) Write short note on CMOS ring oscillator. **07**
OR
- Q.4** (a) Implement logic function $Z = A(D + E) + BC$ using CMOS. **07**
(b) Explain CMOS inverter. **07**
- Q.5** (a) Explain Clocked J-K Latch. **07**
(b) Write VHDL code for 4 X 1 Multiplexer. **07**
OR
- Q.5** (a) Write VHDL code for Half Subtractor. **07**
(b) Explain signal delay in FPGA. **07**

ગુજરાતી

- પ્રશ્ન. ૧ અ VLSI ડિઝાઇન ફ્લો Y- Chart ની મદદ થી સમજાવો. ૦૭
બ ડિઝાઇન ગુણવત્તા સુધારવા માટેના માપદંડ સમજાવો. ૦૭
- પ્રશ્ન. ૨ અ FPGA પર ટ્રૂકનોંધ લખો. ૦૭
બ રેઝિઝ્ટીવ લોડ સાથેનું NMOS ઇનવર્ટર સમજાવો. ૦૭
- અથવા
- બ ડેપ્લેસન લોડ NMOS ઇનવર્ટર સમજાવો. ૦૭
- પ્રશ્ન. ૩ અ CMOS NOR2 ગેટ દોરો અને સમજાવો. ૦૭
બ MOSFET ટ્રાન્ઝીસ્ટર નું ઓપરેશન સમજાવો. ૦૭
- અથવા
- પ્રશ્ન. ૩ અ CMOS NAND2 ગેટ દોરો અને સમજાવો. ૦૭
બ MOS સ્ટ્રક્ચર માટેનો એનર્જી બેન્ડ ડાયાગ્રામ દોરો અને સમજાવો. ૦૭
- પ્રશ્ન. ૪ અ CMOS SR લેચ NAND2 ગેટ ની મદદ દોરો અને સમજાવો. ૦૭
બ CMOS રિંગ ઓસીલેટર પર ટ્રૂકનોંધ લખો. ૦૭
- અથવા
- પ્રશ્ન. ૪ અ $Z = \overline{A(D + E)} + BC$ લોજિક ફંક્શન CMOS ની મદદ થી દોરો. ૦૭
બ CMOS ઇનવર્ટર સમજાવો. ૦૭
- પ્રશ્ન. ૫ અ ક્લોક J-K લેચ સમજાવો. ૦૭
બ 4 X 1 મલ્ટિપ્લેક્સર માટે VHDL કોડ લખો. ૦૭
- અથવા
- પ્રશ્ન. ૫ અ હાફ સબટ્રેક્ટર માટે VHDL કોડ લખો. ૦૭
બ FPGA માં આવતો સીગ્નલ ડીલે સમજાવો. ૦૭
